

S.E. | SEM III (CBGS) - CMPN | INFT

A.M. III

Nov-Dec 2017

Q.P. Code : 23178

[Time: Three Hours]

[Marks: 80]

Please check whether you have got the right question paper.

- N.B: 1. Question No.1 is compulsory.
 2. Attempt any three from the remaining six questions.
 3. Figures to the right indicate full marks.

- a) If the Laplace transform of $\sin^2 3t$ 20
 b) Prove that $f(z) = \log z$ is analytic
 c) Obtain Fourier series for $f(x) = x^2$ in $(-2,2)$
 d) Find the Z-Transform of $\cos 2k, k \geq 0$
- a) Prove that $\bar{F} = 2xyz^3i + x^2z^3j + 3x^2yz^2k$ is irrotational. 06
 Find Scalar potential for \bar{F}
- b) Find the inverse Laplace Transform using Convolution theorem
 $\frac{1}{(s^2+6s+18)^2}$ 06
- c) Find Fourier Series of $f(x) = \frac{\pi-x}{2}$ in $(0, 2\pi)$. 08

Hence deduce that $\frac{\pi}{4} = 1 - \frac{1}{3} + \frac{1}{5} + \dots$

- a) Find the Analytic function $f(z) = u + iv$ if $u + v = \cos x \cosh y - \sin x \sinh y$ 06
 b) Find Inverse Z transform of $\frac{2z^2-10z+13}{(z-3)^2(z-2)}$, $2 < |z| < 3$ 06
 c) Solve the Differential Equation $\frac{d^2y}{dt^2} + 2 \frac{dy}{dx} y = 3te^{-1}$, $y(0) = 4, y'(0) = 2$ using Laplace Transform 08

- Q4 a) Find the Orthogonal Trajectory of $x^2 + y^2 - 3xy + 2y = c$ 06
 b) Using Greens theorem evaluate $\int_C (x^2 - y)dx + (2y^2 + x)dy$, C is closed path formed by $y = 4, y = x^2$ 06

Q.P. Code : 23178

- c) Express the function $f(x) = \begin{cases} \sin x & ; 0 < X \leq \pi \\ 0 & ; X > \pi \end{cases}$ as Fourier Integral. Hence evaluate $\int_0^\infty \frac{\cos(\lambda\pi/2)}{1-\lambda^2} d\lambda$

Q.5

- a) Find Inverse Laplace Transform of $\frac{2s^2-6s+5}{s^3-6s^2+11s-6}$
- b) Find the Bilinear Transformation that maps the points $z = 1, i, -1$ into $w = i, 0, -i$
- c) Evaluate using Stoke's theorem $\int_c \bar{F} \cdot d\bar{r}$ where c is the boundary of the circle $x^2 + y^2 + z^2 = 1, z = 0$ and $\bar{F} = yzi + zxj + xyk$

Q.6

- a) Find the Directional derivative of $\phi = x^2 + y^2 + z^2$ in the direction of the line $\frac{x}{3} = \frac{y}{4} = \frac{z}{5}$ at $(1,2,3)$
- b) Find complex form of Fourier series for $e^{ax}; (-\pi, \pi)$
- c) Find Half Range sine Series for $f(x) = x(2-x) \quad 0 < x < 2$
hence deduce that $\sum \left(\frac{1}{n^2} \right) = \frac{\pi^6}{945}$

Q. P. Code: 26352

(3 Hours)

[Total Marks: 80]

N.B.: (1) Question No. 1 is compulsory.

- (2) Solve any three questions out of remaining five.
- (3) Figures to right indicate full marks.
- (4) Assume suitable data where necessary.

Q1. Solve any four

- a) State ideal and Practical Characteristics of an Op-amp
- b) Explain Multiplexer and Demultiplexer.
- c) Convert following decimal number to Binary, Octal, Hexadecimal and Gray code
 - i) $(128)_{10}$
 - ii) $(73)_{10}$
- d) Explain working of LCD.
- e) Convert D flip flop to S-R flip flop.

20

Q2. a) Implement following using only one 8:1 Multiplexer and few gates.

$$F(A,B,C,D) = \sum m(0,1,3,4,5,8,9,10,12,15)$$

- b) Explain Fixed Biasing Circuit with its stability factor.

10

10

Q3. a) Draw and Explain Instrumentation Amplifier using Op-amp.

10

b) Draw circuit diagram and explain the operation of Monostable Multivibrator using IC555.

10

Q4. a) Minimize the following four variable logic function using K-map and design

10

by using basic gates

$$f(A,B,C,D) = \sum m(0,1,2,3,4,7,8,9,11,15)$$

b) What are the different methods used to improve CMRR in Differential Amplifier.

Explain one in brief.

10

Q5. a) Design a Mod 12 asynchronous counter using J-K-flip flop

10

b) Design 4-bit binary to gray code conversion

10

Q6. Write short notes on any four

20

- a) Explain the working of a Non-inverting amplifier using Op-amp
- b) Explain working of a transistor.
- c) Write VHDL program for NAND gate.
- d) Explain working of Current Mirror Circuit.
- e) Explain block diagram of op-amp.
