

DURATION: 3 HRS.

MAX. MARKS:80

- 1) Question No. 1 is compulsory.
- 2) Attempt any **THREE** of the remaining.
- 3) Figures to the right indicate full marks.

Q.1.A) Determine the constants a, b, c, d, e if

$f(z) = (ax^4 + bx^2y^2 + cy^4 + dx^2 - 2y^2) + i(4x^3y - exy^3 + 4xy)$ is analytic. (5)

B) Find half range Fourier sine series for $f(x) = x^2$, $0 < x < 3$. (5)

C) Find the directional derivative of $\phi(x, y, z) = xy^2 + yz^3$ at the point $(2, -1, 1)$ in the direction of the vector $i + 2j + 2k$. (5)

D) Evaluate $\int_0^\infty e^{-2t} t^5 \cosh t \, dt$. (5)

Q.2.A) Prove that $J_{\frac{3}{2}}(x) = \sqrt{\frac{2}{\pi x}} \left(\frac{\sin x}{x} - \cos x \right)$ (6)

B) If $f(z) = u + iv$ is analytic and $u - v = e^x(\cos y - \sin y)$, find $f(z)$ in terms of z . (6)

C) Obtain Fourier series for $f(x) = x + \frac{\pi}{2} \quad -\pi < x < 0$
 $= \frac{\pi}{2} - x \quad 0 < x < \pi$

Hence deduce that $\frac{\pi^2}{8} = \frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots$ (8)

Q.3.A) Show that $\vec{F} = (2xy + z^3)i + x^2j + 3xz^2k$, is a conservative field. Find its scalar potential and also find the work done by the force \vec{F} in moving a particle from $(1, -2, 1)$ to $(3, 1, 4)$. (6)

B) Show that the set of functions $\{\sin(2n+1)x\}$, $n = 0, 1, 2, \dots$ is orthogonal over $[0, \pi/2]$. Hence construct orthonormal set of functions. (6)

[TURN OVER]

C) Find (i) $L^{-1}\{\cot^{-1}(s+1)\}$

$$(ii) L^{-1}\left(\frac{e^{-2s}}{s^2+8s+25}\right) \quad (8)$$

Q.4) A) Prove that $\int J_3(x) dx = -\frac{2J_1(x)}{x} - J_2(x)$ (6)

B) Find inverse Laplace of $\frac{s}{(s^2+a^2)(s^2+b^2)}$ ($a \neq b$) using Convolution theorem. (6)

C) Expand $f(x) = x \sin x$ in the interval $0 \leq x \leq 2\pi$ as a Fourier series.

$$\text{Hence, deduce that } \sum_{n=2}^{\infty} \frac{1}{n^2-1} = \frac{3}{4} \quad (8)$$

Q.5) A) Using Gauss Divergence theorem evaluate $\iint_S \vec{N} \cdot \vec{F} ds$ where $\vec{F} = x^2\vec{i} + z\vec{j} + yz\vec{k}$

and S is the cube bounded by $x=0, x=1, y=0, y=1, z=0, z=1$ (6)

B) Prove that $J_2'(x) = \left(1 - \frac{4}{x^2}\right)J_1(x) + \frac{2}{x}J_0(x)$ (6)

C) Solve $(D^2+3D+2)y = 2(t^2+t+1)$, with $y(0)=2$ and $y'(0)=0$ (8)
by using Laplace transform

Q.6) A) Evaluate by Green's theorem for $\int_C (e^{-x} \sin y dx + e^{-x} \cos y dy)$ where C is the (6)
the rectangle whose vertices are $(0,0), (\pi, 0), (\pi, \pi/2)$ and $(0, \pi/2)$

B) Show that under the transformation $w = \frac{z-i}{z+i}$, real axis in the z -plane is mapped onto the (6)
circle $|w| = 1$

C) Find Fourier Sine integral representation for $f(x) = \frac{e^{-ax}}{x}$ (8)

---X---X---X---

(3 Hours)


[Total Marks : 80

- N.B. :** (1) Question No. 1 is compulsory.
 (2) Attempt any three questions out of remaining five questions.
 (3) Assume suitable data if required and mention the same in answer sheet.


I. Attempt any five questions

20

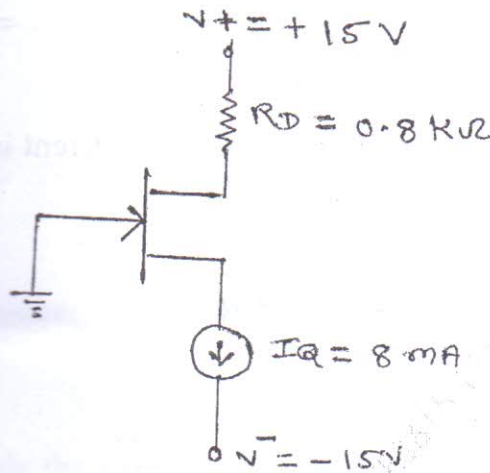- (a) For the circuit given below, the transistor parameters are $V_p = -3.5\text{V}$, $I_{DSS} = 18\text{mA}$ and $\lambda = 0$. Calculate V_{GS} and V_{DS} .



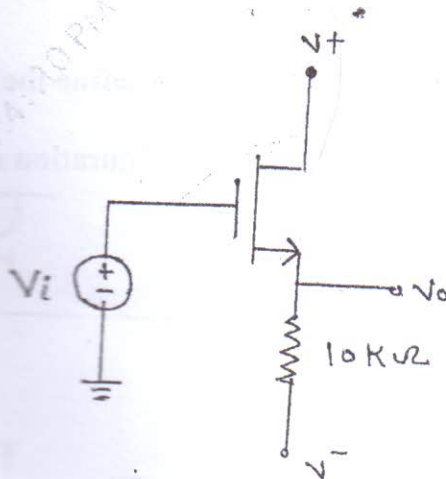
- (b) The small-signal parameters of the NMOS transistor in the source follower circuit shown in fig. below are $g_m = 5\text{mA/V}$ and $r_o = 100\text{ k}\Omega$. Determine the voltage gain and output resistance.




[TURN OVER]

2

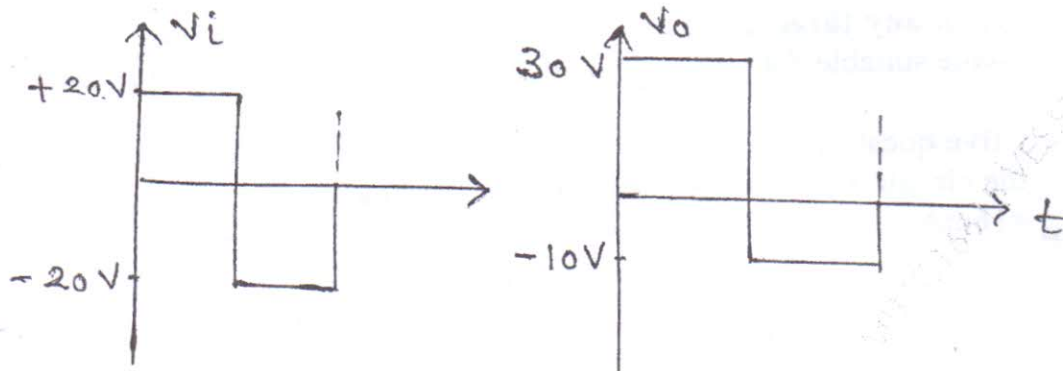- (c) Design a diode clamper to generate a steady-State output voltage V_o from the input voltage V_i in fig. Shown below if diode is Ideal.



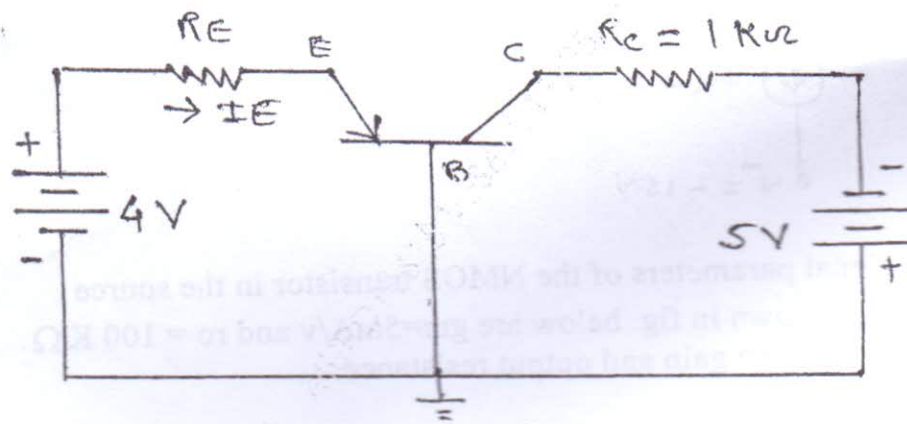- (d) For the circuit shown, determine R_E such that the emitter current is limited to $I_E = 1mA$, Also find I_B (Given $\alpha = 0.9920$)




- (e) Describe the channel length modulation effect and define the parameters λ .
- (f) Draw a neat circuit diagram of emitter follower configuration and its hybrid - π model.

[TURN OVER]

2 (a) Determine the following for the network given below

10

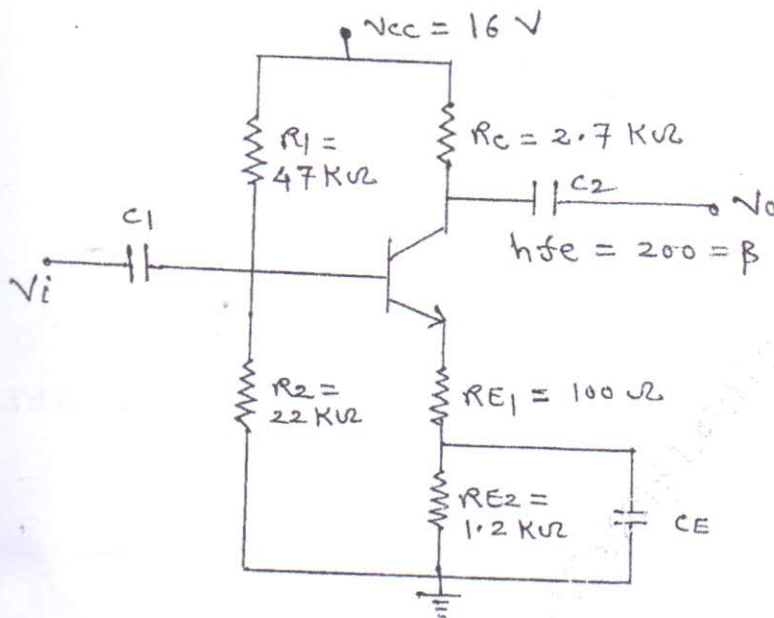- (i) Q- Point
(ii) A_v , A_i , Z_i , Z_o .




(b) Explain the working of Wein Bridge oscillator. Derive the expression for frequency of oscillation and condition of oscillation.


10

3 (a) Draw output waveform for clipper and clamper circuits shown.

10

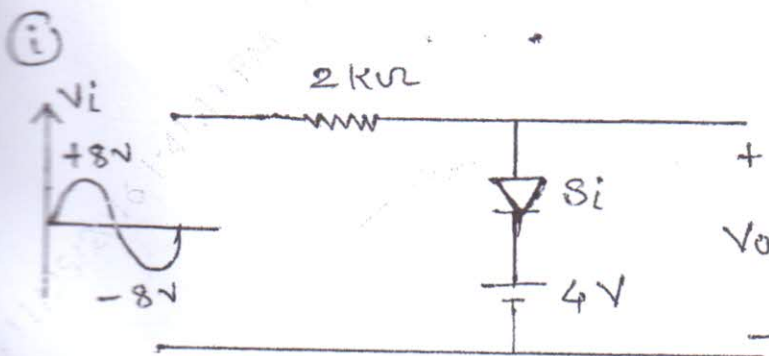


[TURN OVER]

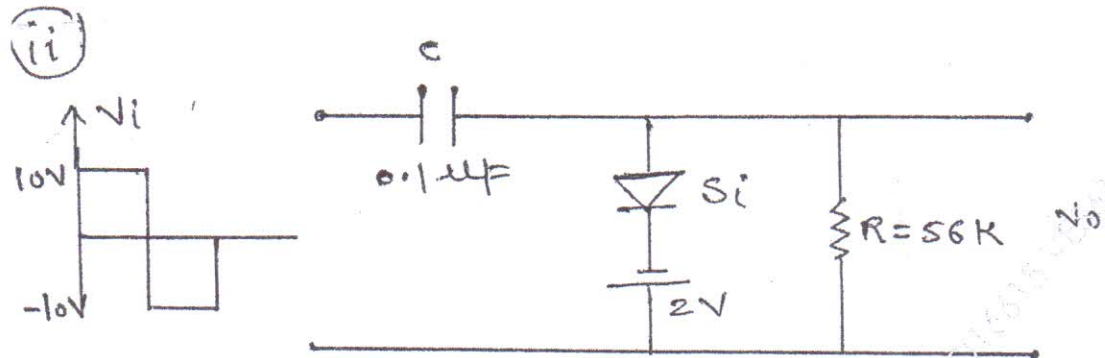

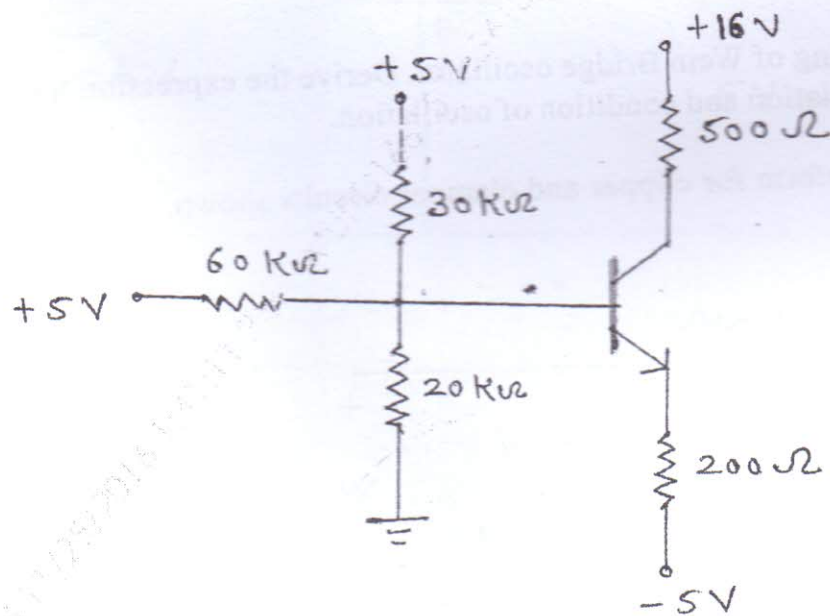
(b) Explain construction and characteristics of n-channel Depletion MOSFET. Draw transfer characteristics and drain characteristics. 10

4 (a) Find I_{CQ} and V_{CEQ} for the circuit shown in figure if $\beta = 100$ 10



[TURN OVER]

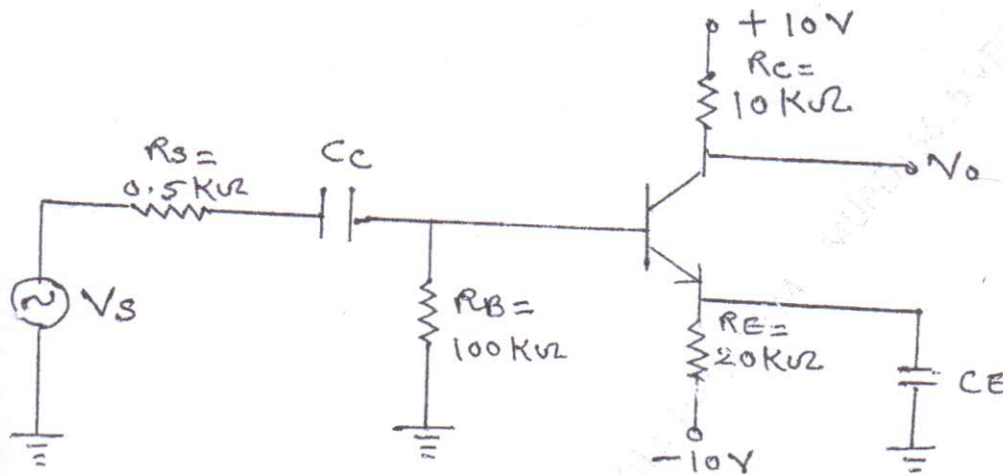
- (b) For the circuit in fig. let $\beta = 100$, $V_A = 100V$, $V_{BE}(\text{on}) = 0.7V$. Determine 10
- Small signal voltage gain
 - Input resistance seen by the signal source
 - output resistance



- 5 (a) For the amplifier circuit shown below

10

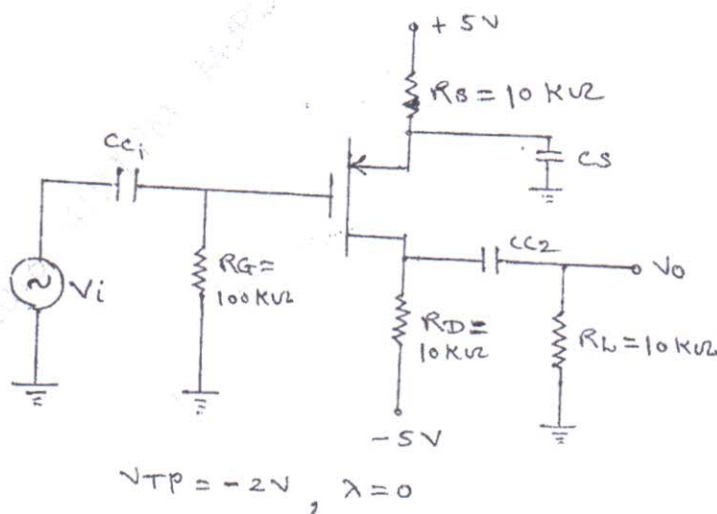- Determine the values of K_p such that $V_{SDQ} = 6V$
- Determine the resulting value of I_{DQ} and small signal voltage gain.



[TURN OVER]

- (b) Draw circuit diagram of common source amplifier with voltage divider bias with unbypassed source resistance ' R_s ' using n-channel EMOSFET. Derive expression for voltage gain, input resistance and output resistance.

6. Write short note on **any four** :-

- (i) Energy band diagram of MOS capacitor
- (ii) Construction and operation of Schottky diode
- (iii) Crystal Oscillator
- (iv) Hybrid parameters
- (v) Stability factor of biasing circuit.

(3 Hours)


[Total Marks : 80

- N.B. :** (1) Question No. 1 is compulsory.
(2) Attempt any 3 questions from Q.2 to Q.6.
(3) Figures to the **right** in the bracket indicate **full** marks.
(4) Assume suitable data if necessary.


- | | | | |
|----|----|---|----|
| 1. | a) | State basic theorems of Boolean algebra. | 5 |
| | b) | Compare Mealy and Moore machine | 5 |
| | c) | Define Noise Margin, Propagation delay, Power Dissipation | 5 |
| | d) | Design a full adder using half adders and logic Gates | 5 |
| 2. | a) | Prove that NAND and NOR Gates are universal Gates | 10 |
| | b) | Design a 2-bit comparator and implement using logic Gates | 10 |
| 3. | a) | Design a 4 bit Binary to Grey code converter. | 10 |
| | b) | Implement the given function using single 4:1 Multiplexer and few logic gates: $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13, 15)$ | 10 |
| 4. | a) | What is a universal shift register? Explain its various modes of operation | 10 |
| | b) | Write a VHDL program to design a 3:8 Decoder. | 10 |
| 5. | a) | Minimize the following expression using Quine McClusky Technique
$F(A,B,C,D) = \sum m(0,1,2,3,5,7,9,11)$ | 10 |
| | b) | Convert JK FF to T FF and JK FF to D FF | 10 |
| 6. | a) | Explain the working of 3-bit asynchronous counter with proper timing diagram. | 10 |
| | b) | Write a note on CPLDs. | 10 |
-

- N. B. :** (1) Question No. 1 is **compulsory**.
(2) Attempt any **three** questions from the remaining **five**.
(3) **Figures** to the **right** indicate **full marks**.
(4) Use Smith chart for transmission line problem.
(5) Assume suitable data if required.

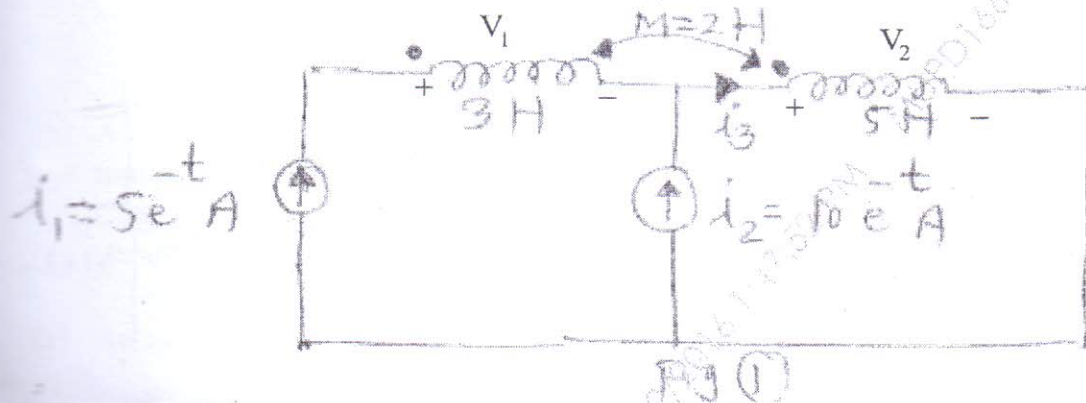
- I. (a) In the network shown in fig. (1), find the voltages V_1 and V_2 . 5



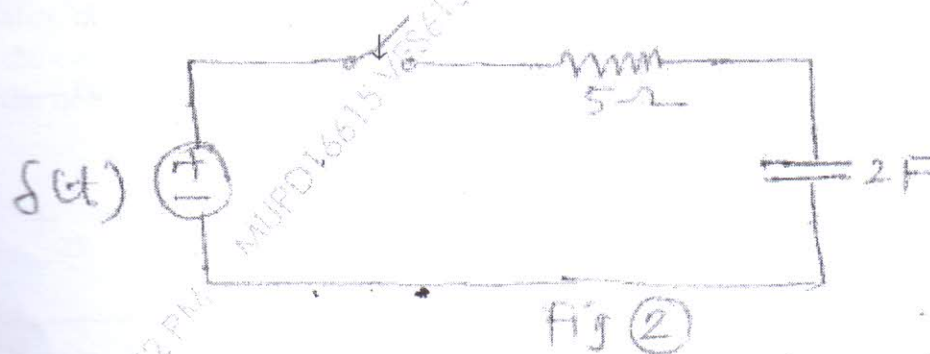- (b) For the network shown in fig (2), determine the current $i(t)$ when the switch is closed at $t = 0$ with zero initial conditions. 5



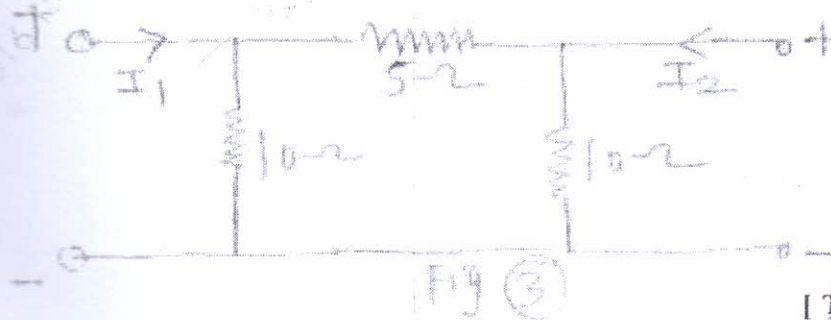- (c) Find the lattice equivalent of symmetric π -network shown in figure (3). 5



[TURN OVER

(d) Define the following parameters of transmission line.

- (i) Input impedance
- (ii) Characteristics impedance
- (iii) VSWR
- (iv) Reflection coefficient
- (v) Transmission coefficient

5

2. (a) In the network shown in fig. (4) the switch closes at $t = 0$. The capacitor has no initial charge. Find $V_C(t)$ and $i_C(t)$. 10

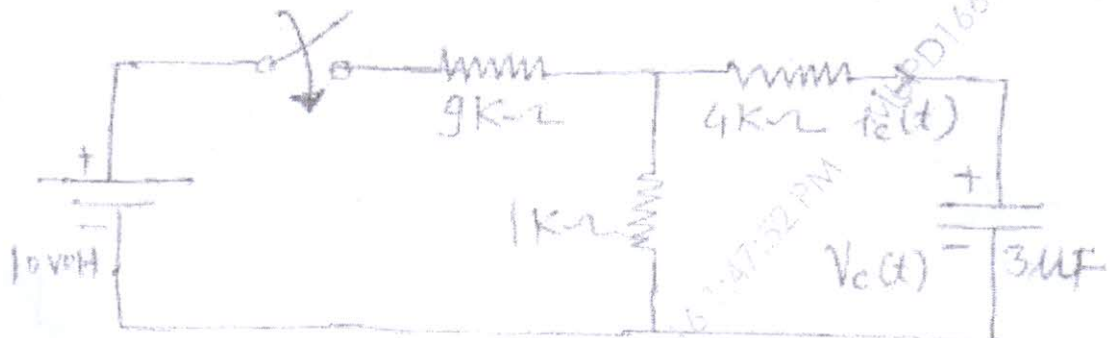


Fig (4)

- (b) Determine the transmission parameters of the network shown in fig (5) using the concept of inter connection of two port network. 10


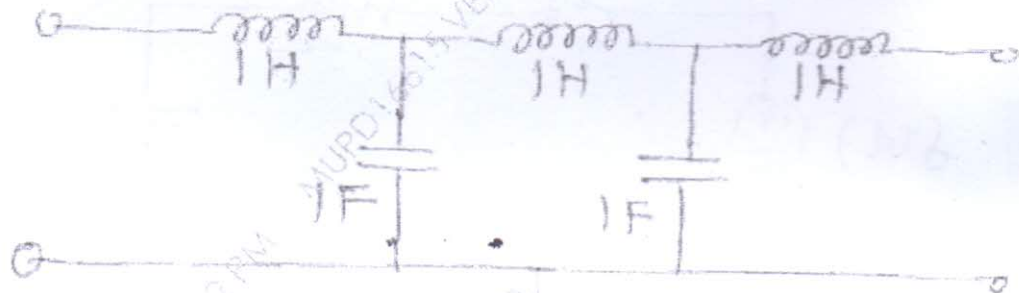


Fig (5)

[TURN OVER

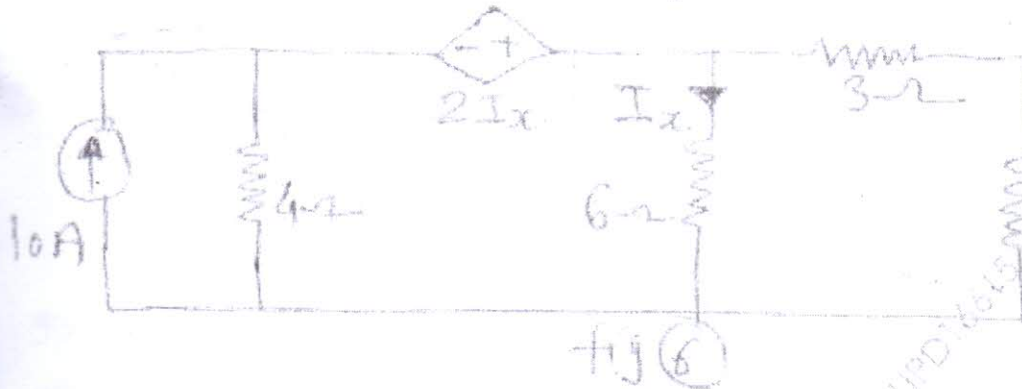3. (a) For the network shown in fig (6), calculate the maximum power that may be dissipated in the load resistor R_L . 10




- (b) A load impedance $Z_L = (30 + j60)\Omega$ is connected to a 50Ω transmission line of 2 cm length and operated at 2 GHz. Using Smith Chart, find the input impedance of transmission line under the assumption that phase velocity is 50% of speed of light. 10

4. (a) An impedance is given by- 10

$$Z(s) = \frac{8(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$


Realise the network in Foster-I and Cauer-I form

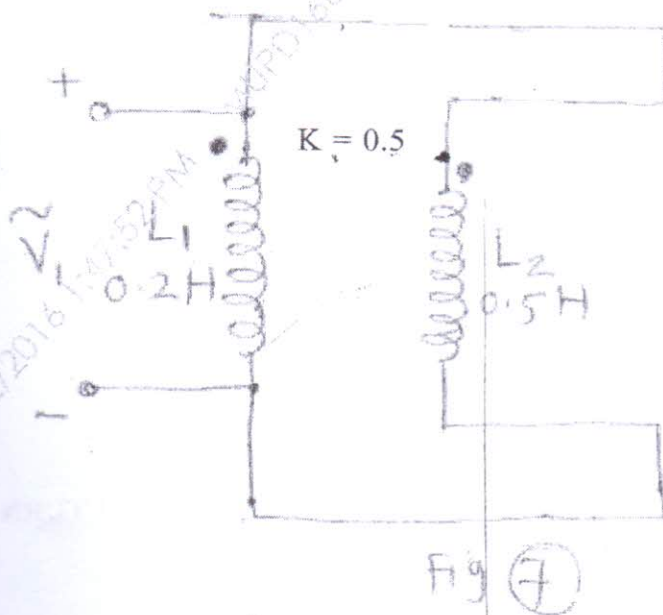- (b) In the coupled circuit of figure (7), find the input impedance as well as the net inductance. 10



[TURN OVER]

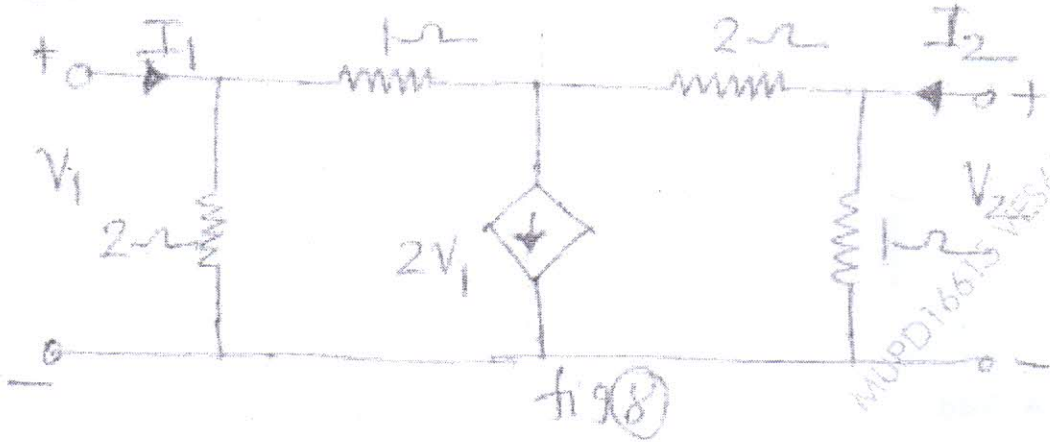5. (a) Find the open circuit impedance parameters of the circuit shown in fig. (8). Also find the Y parameters. 10




- (b) (i) State properties of LC driving point impedance functions. 5
 (ii) Test whether the polynomial is Hurwitz 5
 $P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$

6. (a) A co-axial line has the following parameters 10
 $R = 6 \Omega/\text{m}$
 $L = 5.2 \times 10^{-8} \text{ H/m}$
 $G = 6 \times 10^{-3} \text{ mho/m}$
 $C = 2.136 \times 10^{-10} \text{ F/m}$
 $f = 1 \text{ GHz}$
 $Z_L = (100 + j 100) \Omega$
 Compute the following parameter using formulae
 (i) Characteristics impedance
 (ii) Propagation constant
 (iii) Reflection coefficient at the load
 (iv) Transmission coefficient at the load

[TURN OVER

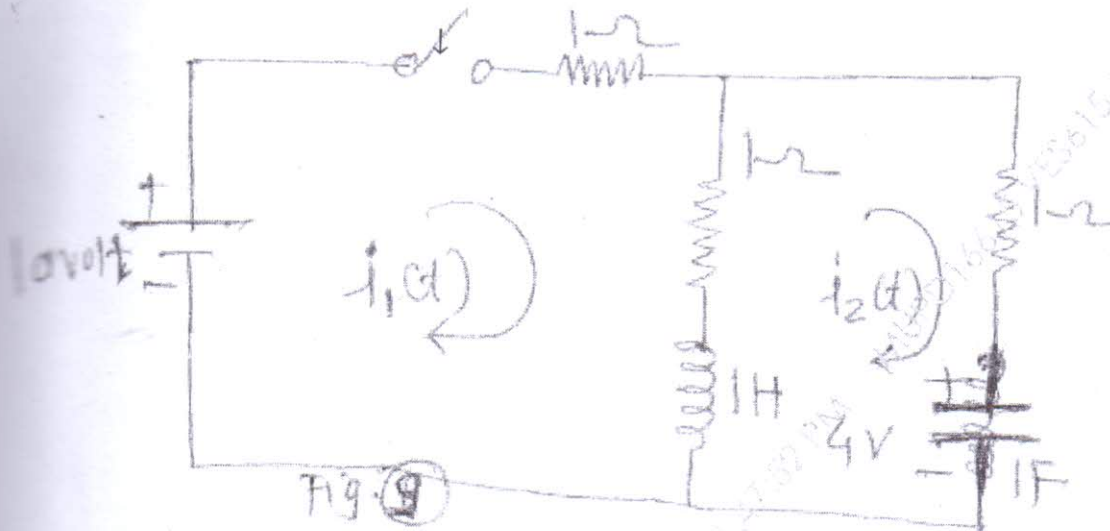- (b) In the network shown in fig (9), the switch is closed at $t = 0$. Find the current $i_1(t)$ and $i_2(t)$ when initial current through the inductor is zero and initial voltage is 4 volt. 10



Q.P. Code : 545500

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Attempt **four** questions, question no **1** is **compulsory**.
(2) Assume suitable data where ever required.
(3) Answers to the questions should be grouped together.
(4) Figure to the **right** of question indicates **full** marks.

1. Attempt any four :

20

- (a) Significance of three and half digit display
- (b) Define accuracy, precision and sensitivity with suitable example
- (c) Explain working of strain gauge and its application in load measurement
- (d) List various sensors for pressure and temperature along with their ranges
- (e) A galvanometer, with a 1 mA full scale deflection and an internal resistance of 500Ω , is to be used as voltmeter, find series resistance for 1V and 10 V ranges.

- 2. (a)** Draw and explain working of capacitive transducer for level measurement. **10**
(b) Draw neat block diagram of CRO and explain its functioning, comment on role of sweep in CRO. **10**

- 3. (a)** Draw and explain R-2R ladder network DAC for 3 bits input taking suitable example. **10**
(b) Explain Kelvin's double bridge and its application in very low resistance measurement. **10**

- 4. (a)** Explain SAR OR Flash type ADC with the help of block diagram and comment on its speed. **10**
(b) Explain LVDT and define its application in displacement measurement. **10**

- 5. (a)** Explain Heterodyne type waves analyser and its applications. **10**
(b) Discuss DSO with the help of block diagram along with various modes of operation also explain its applications. **10**

- 6. (a)** Draw and discuss Hey Bridge and its application for measurement of inductance. **10**
(b) Define power and energy and explain working of an energy meter. **10**