

(3 hours)

Total Marks-80

N.B. 1) Question No.1 is compulsory.

2) Attempt any THREE questions from Q.No.2 to Q.No.6

3) Figures to the right indicate full marks

- Q1) a) Find $L\left[\frac{\cos 2t \sin t}{e^t}\right]$ [5]
- b) Determine the constants a,b,c,d if $f(z) = x^2 + 2axy + by^2 + i(cx^2 + 2dxy + y^2)$ is analytic. [5]
- c) Find Half range cosine series for $f(x) = x(\pi - x), 0 < x < \pi$ [5]
- d) Find the directional derivative of $f(x, y, z) = xy^2 + yz^3$ at the point (2,-1,1) in the direction of the vector $i + 2j + 2k$ [5]
- Q2) a) Show that the function $u = 3x^2y + 2x^2 - y^3 - 2y^2$ is harmonic. [6]
Find its harmonic conjugate and corresponding analytic function.
- b) Find the Fourier series for $f(x) = 1 - x^2$ in $(-1,1)$. [6]
- c) Find i) $L^{-1}\left[\frac{e^{-\pi s}}{s^2 - 2s + 2}\right]$ [8]
ii) $L^{-1}\left[\tan^{-1}\left(\frac{s+a}{b}\right)\right]$
- Q3) a) Find the angle between the surfaces $x \log z + 1 - y^2 = 0,$ [6]
 $x^2y + z = 2$ at (1,1,1)
- b) Prove that $J'_2(x) = \left(1 - \frac{4}{x^2}\right)J_1(x) + \frac{2}{x}J_0(x)$ [6]

c) Obtain Fourier series for

[8]

$$f(x) = \begin{cases} x + \frac{\pi}{2} & , -\pi < x < 0 \\ \frac{\pi}{2} - x & , 0 < x < \pi \end{cases}$$

Hence deduce that $\frac{\pi^4}{96} = \frac{1}{1^4} + \frac{1}{3^4} + \dots$

Q4) a) Using Gauss's Divergence theorem, prove that

[6]

$\iint_S (y^2 z^2 i + z^2 x^2 j + z^2 y^2 k) \cdot \bar{N} ds = \frac{\pi}{12}$ where S is the part of the sphere $x^2 + y^2 + z^2 = 1$ above the xy-plane.

b) Prove that $J_{-\frac{1}{2}}(x) = \sqrt{\frac{2}{\pi x}} \cdot \cos x$

[6]

c) Solve using Laplace Transform $(D^2 + 2D + 5)y = e^{-t} \sin t$, when $y(0) = 0, y'(0) = 1$

[8]

Q5) a) Find inverse Laplace Transform using convolution theorem for

[6]

$$\frac{1}{(s-a)(s+a)^2}$$

b) Prove that $J_3(x) + 3J_0(x) + 4J_0'''(x) = 0$

[6]

c) Obtain the complex form of Fourier Series for $f(x) = e^{ax}$ in $(-l, l)$

[8]

Q6) a) Using Green's Theorem in the plane evaluate

[6]

$\oint (x^2 - y) dx + (2y^2 + x) dy$ around the boundary of the region defined by $y = x^2, y = 4$

b) Show that the map of real axis of the Z-plane is a circle under the

[6]

transformation $w = \frac{z}{z+i}$. Find its centre and the radius.

c) Find Fourier Integral Representation for

[8]

$$f(x) = \begin{cases} 1 - x^2 & \text{for } |x| \leq 1 \\ 0 & \text{for } |x| > 1 \end{cases}$$

Choice /

(3 Hours)

(Total Marks : 80)


Please check whether you have got the right question paper.

- NB:**
- 1) Question No. 1 is compulsory.
 - 2) Solve any three questions from the remaining five questions.
 - 3) Figures to the right indicate full marks.
 - 4) Assume suitable data if necessary and mention the same in answer sheet.

1. Attempt any Four questions :

(20)

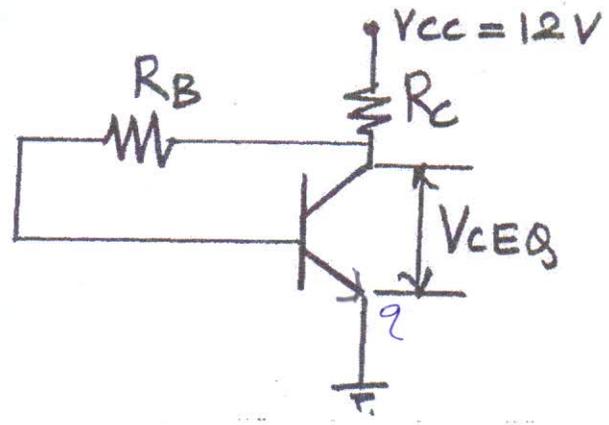- a) Explain Various types of Resistors.
- b) Give the equation for the current in semiconductor diode. With the help of this equation explain in detail the V-I characteristics of a semiconductor diode.
- c) Explain Zener as a Voltage regulator.
- d) Find Values for R_B and R_C :



$P_{dc} = 120$
 $V_{CEQ} = 5V$
 $I_{CQ} = 5mA$
 - 0m

- e) Compare BJT CE Amplifier and JFET CS Amplifier.
- f) Draw and explain high frequency model of BJT for CE configuration.

2. Design a single stage CE amplifier suitable for low frequencies up to 10Hz to give (20)

voltage gain $A_v \geq 70$ and the output voltage of 4.5 Volts; employing transistor type BC147A. Calculate the expected A_v and maximum output voltage with negligible distortion that can be obtained from the designed circuit. Also, calculate the input resistance of the amplifier. Specify clearly the supply voltage V_{CC} for the designed circuit.

$V_{CEQ} < V_{CC}$
 ?

3. a) A dc voltage of 350 Volts with peak ripple voltage not exceeding 5 Volts is (10)

required to supply a 500 Ω load. Determine following if inductor filter and full wave rectifier is used

- 1) Inductance required
- 2) Input voltage required.

b) Explain and derive the expression for ripple factor for capacitor filter with full (10) wave rectifier.


BC147A
 $h_{ie} = 2.7K$
 $h_{re} = 1.5 \times 10^{-4}$
 $h_{te\ min} = 125$

$h_{te\ type} = 220$
 $h_{FE\ min} = 115$
 $h_{FE\ type} = 180$
 $h_{oe} = 18 \mu A$


9920055296

$h_{te\ max} = 260$

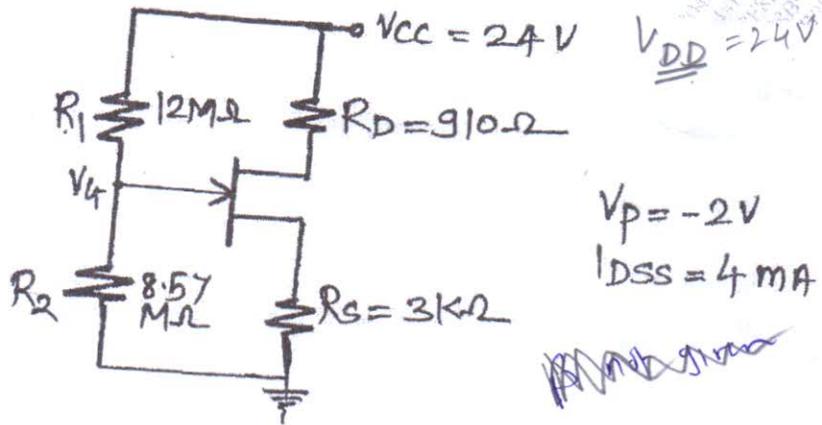4. a) For the circuit shown below determine I_{DQ} and verify if the FET will operate in pinch off region : (10)



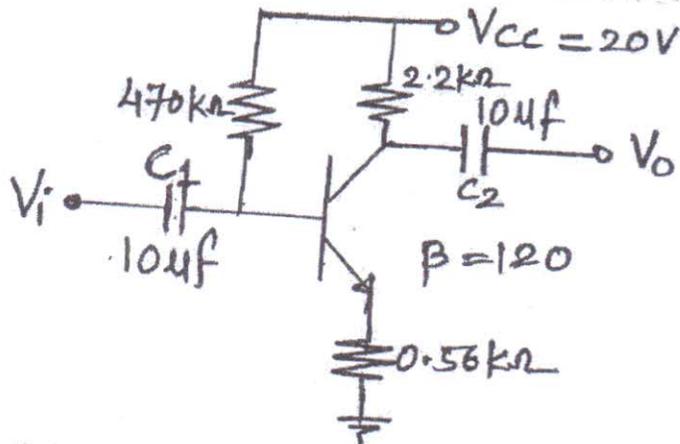- b) State and explain Miller theorem. (10)
5. a) Determine Z_i , Z_o and A_v for the circuit shown below : (10)



- b) Draw small Signal hybrid parameter equivalent circuit for CE amplifier and define the same. What are the advantages of h-parameters? (10)

6 Write short note on :

- Hybrid Parameter
- Regions of operation of FET
- Stability factor of biasing circuits
- DC load line concept in BJT. Why Q point should be at the middle of load line and fixed?

वॉल्टेज गेन
 i/p पंचेन (20)

Transistor type	P _{max} @ 25°C Watts	I _{max} @ 25°C Amps	V _{GS} max volts d.c.	V _{GS} (Stat) volts d.c.	T _{max} °C	D.C. current gain		Signal amp.	Derate above 25°C W/°C							
											min	typ.			max.	typ.
2N 3055	115-3	15-0	1-1	100	60	70	90	7	200	20	50	70	15	120	1-5	0-7
ECN 055	30-0	5-0	1-0	60	30	55	60	5	200	25	50	100	25	125	1-5	0-4
ECN 149	30-0	4-0	1-0	50	40	—	—	8	150	30	50	110	33	115	1-2	0-3
ECN 100	5-0	0-7	0-6	70	60	65	—	6	200	50	90	280	50	200	0-9	0-05
BC147A	0-25	0-1	0-5	30	45	50	—	6	125	115	180	220	125	200	0-9	—
2N 525(PNP)	0-25	0-5	0-5	35	30	—	—	—	100	35	—	65	—	—	—	—
BC147B	0-25	0-1	0-5	50	45	50	—	6	125	200	200	450	240	500	0-9	—

Transistor type	h _{ie}	h _{re}	h _{fe}	g _m
BC 147A	2-7 K Ω	10 μ V	15 × 10 ⁻⁴	0-4°C/mW
2N 525 (PNP)	1-4 K Ω	25 μ V	12 × 10 ⁻⁴	—
BC 147B	4-5 K Ω	30 μ V	2 × 10 ⁻⁴	0-4°C/mW
ECN 100	500 Ω	—	—	—
ECN 149	250 Ω	—	—	—
ECN 055	100 Ω	—	—	—
2N 5055	25 Ω	—	—	—

BFV 11--JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	I _D 0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0	3-5	4-0
I _D max. mA	10	9-0	8-3	7-6	6-8	6-1	5-4	4-3	3-1	2-2	2-0	1-1	0-5	0-0
I _D typ. mA	7-0	6-0	5-4	4-6	4-0	3-3	2-7	1-7	0-7	0-2	0-0	0-0	0-0	0-0
I _D min. mA	4-0	3-0	2-2	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0

N-Channel JFET

Type	V _{GS} max. Volts	V _{GS} max. Volts	V _{GS} max. Volts @ 25°C	P _D max. @ 25°C	I _D max.	f _{max} (typical)	τ _s	Derate above 25°C	g _m		
2N5822	50	50	50	300 mW	175°C	2 mA	3000 μs	6	50 KΩ	2 mW/°C	0-59°C/mW
BFV 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μs	2-5	50 KΩ	—	0-59°C/mW

h_{fe}
(hFE captr m)

- Q.5 (A) With neat diagram, explain the working of Universal Shift Registers. Give its applications. (1)
- (B) Analyze the circuit given in Figure 5(B). Assume initial state as $A=0, B=0$. Complete a state table that shows the behavior of this state machine. Is this a Moore or Mealy machine? (Explain with a sentence) (1)


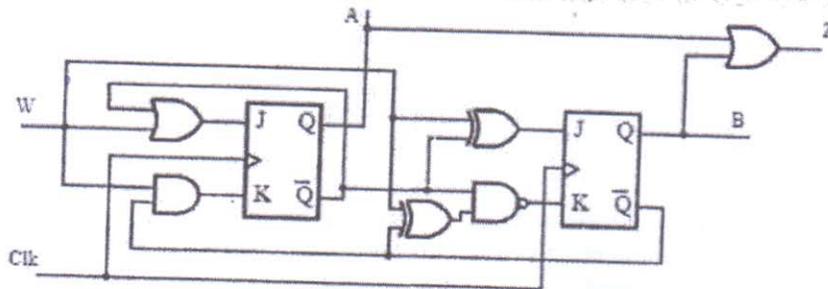


Fig 5(B)


6. (A) Convert T type flip flop into D type flip flop. (05)
- (B) Compare Moore with Mealy circuits. (05)
- (C) Compare PAL with PLA. (05)
- (D) Compare FPGA with CPLD. (05)

1. Question no.1 is compulsory.
 2. Attempt any three from remaining 5 questions.

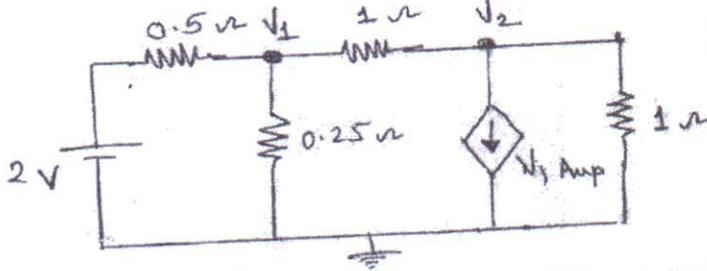
a) Determine the node voltages V_1 and V_2 by Nodal Analysis. 5



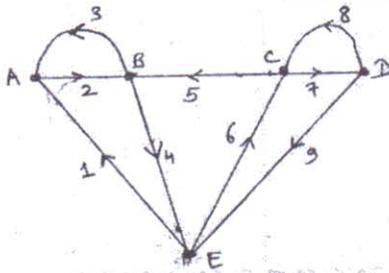b) Find incidence Matrix (A) for the graph shown in figure. 5



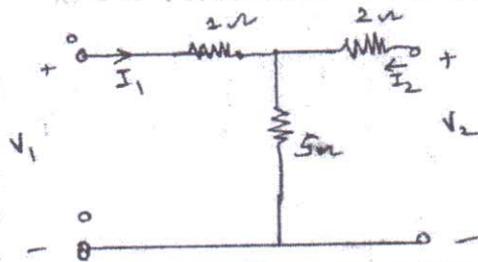
c) Find the transmission parameters [A, B, C, D] for the network shown in the fig. 5



d) Test whether $F(s)$ is a positive real function 5


$$F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$

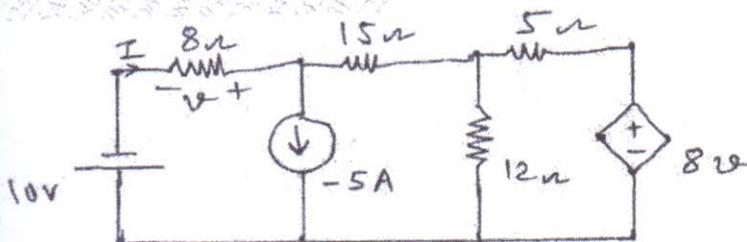a) Find the current 'I' in 8Ω resistor by superposition theorem. 10




- Paper / Subject Code: 51204 / Circuit Theory and Networks
- b) The switch in the circuit shown is changed from position '1' to position '2' at $t=0$. Steady state conditions having reached before switching. Find the values of
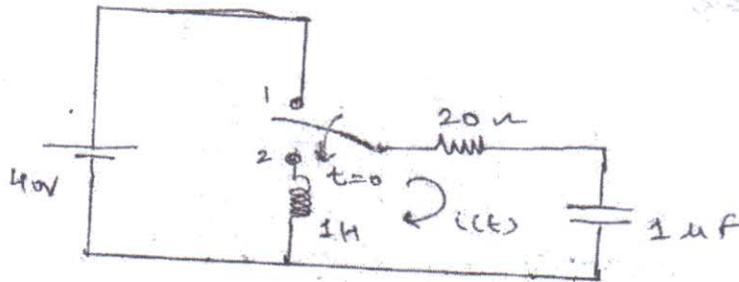
$$i, \frac{di}{dt} \text{ and } \frac{d^2i}{dt^2} \text{ at } t = 0^+$$



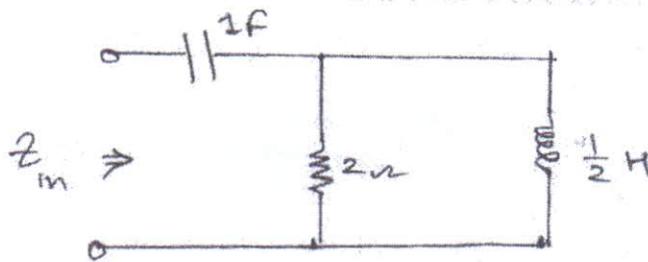
- c) Determine the driving point impedance function $z_{in}(s)$ for the Network shown in fig. and also draw pole-zero plot.




- Q3 a) Synthesize $z(s)$ into Foster -I and cauer-I forms.

$$z(s) = \frac{s^2 + 12s^2 + 32s}{s^2 + 7s + 6}$$

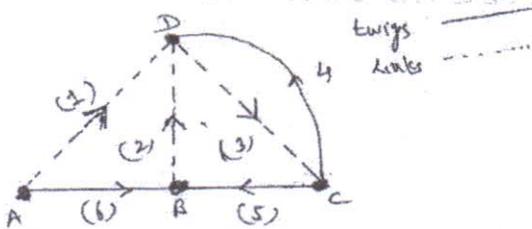
- b) Determine f-loop matrix for the graph shown in fig.




- c) Find voltage across 2Ω resistor.

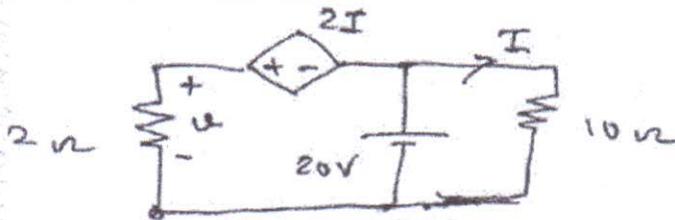

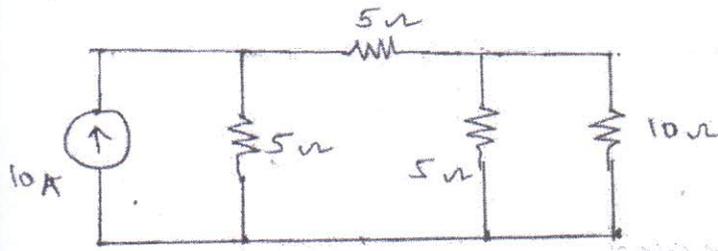
- a) Write f-cut set matrix for the circuit shown and hence obtain matrix Node equation using Graph Theory. 10



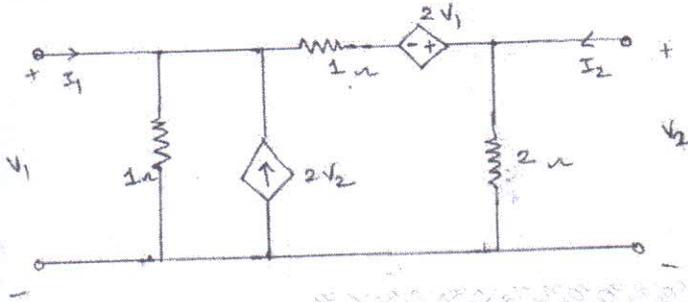- b) For the Network shown in the figure determine z and y parameters. 10




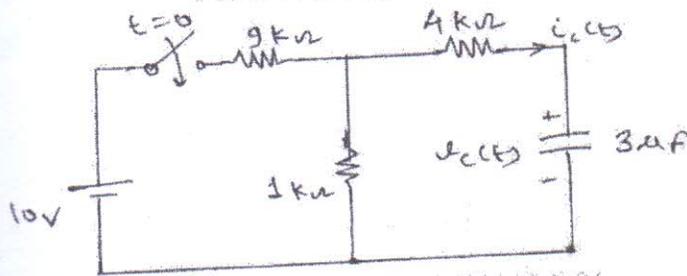- a) In the figure shown the switch is closed at $t=0$ with no initial charge on the capacitor. Determine $v_c(t)$ and $i_c(t)$ for $t \geq 0$. 10




- b) Test the following for Hurwitz polynomial
- i. $P(s) = s^6 + 3s^5 + 8s^4 + 15s^3 + 17s^2 + 12s + 4$
 - ii. $P(s) = s^5 + s^3 + s$

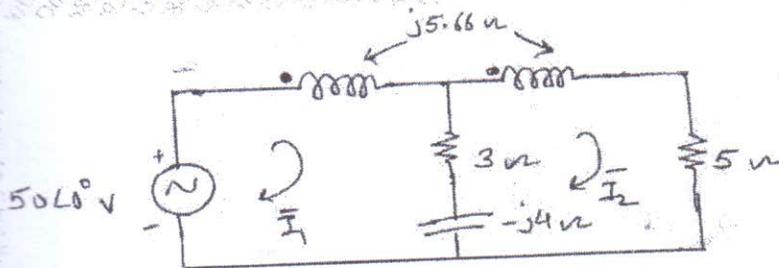
- c) Write Mesh equations for the magnetically coupled circuit shown in fig. 5



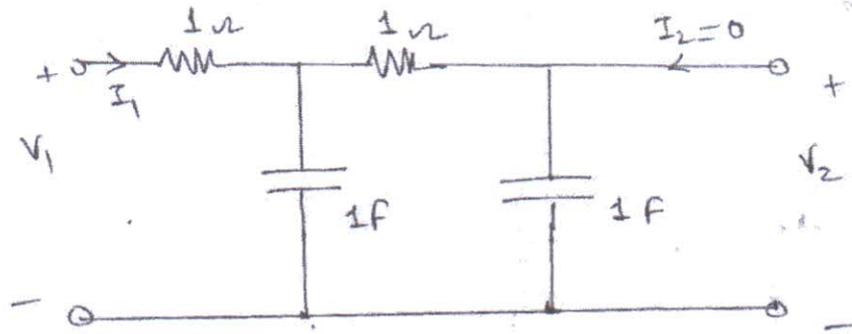Q6 a) Paper / Subject Code: 51204 / Circuit Theory and Networks
 Determine $\frac{I_2}{I_1}$, $\frac{V_2}{V_1}$ for the network shown in the figure.



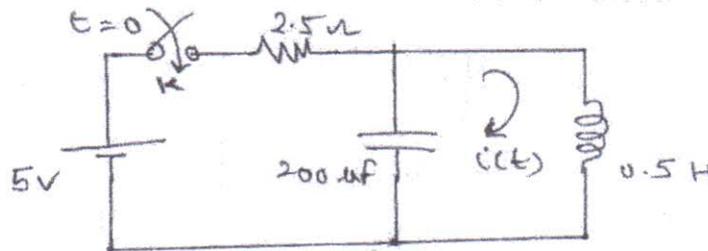b) For the circuit shown in the figure, the switch 'K' is closed at $t=0$ and steady state is attained before closing the switch. By using 'Laplace Transform' techniques determine $i(t)$ for $t \geq 0$.



c) Derive the condition of Reciprocity and symmetry for ABCD parameters.

EIC (3hours)

Q.P Code:


N.B:

- (1) Attempt four questions, question no:1 is Compulsory.
- (2) Assume suitable data wherever required.
- (3) Answers to the questions should be grouped together.
- (4) Figure to the right of question indicates full marks.

1. Attempt all:

20M

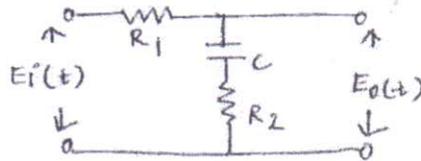
- (a) Derive an expression for the resistance using Wheatstone bridge for balanced condition
- (b) Find the transfer function of the given electrical network



- (c) Explain various criteria for selection of transducers
- (d) Compare analog and digital Data Acquisition system.
- (e) Check whether the given system is stable
 $s^5 + s^4 + 2s^3 + 2s^2 + 3s + 15 = 0$

2.

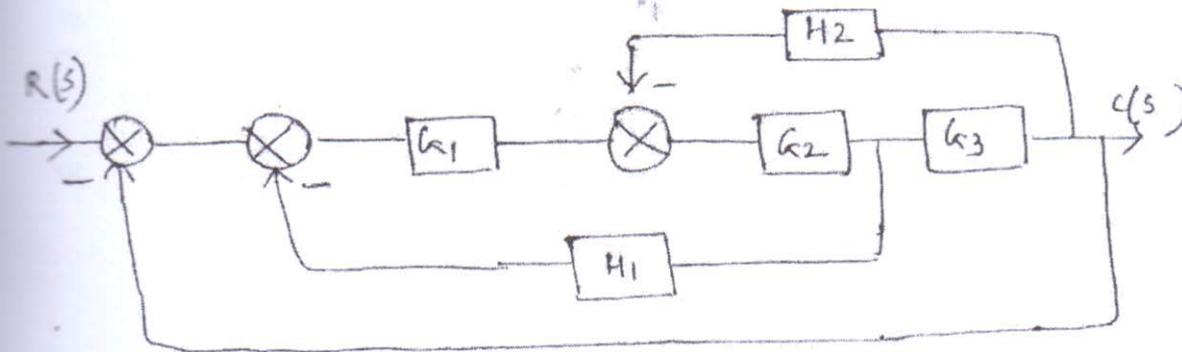- (a) Describe how Q meter is used for measurement of low impedance. Also List the various sources of errors in Q meter. 10
- (b) Using Block diagram reduction techniques, find closed loop transfer function 10



3


- (a) Sketch the root locus of a unity feedback control system with $G(s) = \frac{k}{s(s+4)(s+6)}$ and determine the value of k for marginal stability 10
- (b) A Unity feedback control system has $G(S) = \frac{10}{s(1+0.4s)(1+0.1s)}$, $H(s)=1$ 10
 Draw the bode plot and predict stability

4

- (a) Explain basic telemetry system. 05
- (b) For Unity Feedback system $G(s) = \frac{k}{s(1+0.4s)(1+0.25s)}$, find range of K, marginal value of K and frequency of sustained oscillation. Using Routh's criterion. 05
- (c) Explain with neat diagram working principle of LVDT and Explain advantages and disadvantages of LVDT 10

5

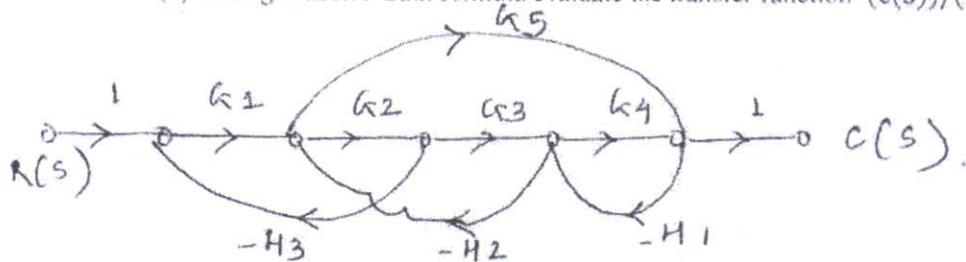- (a) Using Mason's Gain formula evaluate the transfer function $(c(S))/(R(s))$ 10



- (b) Explain Kelvin's double Bridge and its application for measurement of low resistance and derive expression for unknown resistance. 10

6

- (a)
- (i) Compare the temperature transducers with respect to their characteristics and measurement range 05
- (ii) How stability of the system can be analyzed using Nyquist criterion 05
- (iii) Explain Digital Data Acquisition system 05
- (iv) A unity feedback system has open loop transfer function as $\frac{(1+0.4s)}{s(s+0.6)}$. Obtain Unit step Response, Rise Time and Peak overshoot 05