

(Time: 3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is compulsory.
 (2) Solve any three questions out of remaining five.
 (3) Figures to right indicate full marks.
 (4) Assume suitable data where necessary.

Q1. Solve any four 20

- Explain DC operating point and its variation with the help of output characteristics of transistor.
- Convert S-R flip flop to J-K flip flop.
- Design Ex-OR gate using NAND and NOR gates.
- Design full subtractor using half subtractor and additional gates.
- Convert following decimal number to Binary, Octal, Hexadecimal and Gray code
 i) $(345)_{10}$ ii) $(818)_{10}$

Q2. a) Explain collector to base bias Circuit with its stability factor. 10

- b) Minimize the following four variable logic function using K-map and Design using only NAND gates. 10

$$f(A,B,C,D) = \sum m(0,1,2,3,5,8,9,10,11,12,14)$$

Q3. a) Design 4-bit binary to gray code conversion using basic gates. 10

- b) i) Implement following using only one 8:1 Multiplexer and few gates.

$$F(A,B,C,D) = \sum m(1,3,4,5,8,9,12,15)$$

- ii) With neat logic diagram explain in short operation of Universal Shift Register. 10

Q4. a) Design a Mod 10 synchronous counter using J-K Flipflop. 10

- b) Using Quine MC Cluskey Method determine Minimal SOP form for 10

$$F(A,B,C,D) = \sum m(0,1,2,5,6,7,8,9,10,14)$$

Q5. a) Explain about ENTITY declarations in VHDL and write VHDL program for NAND and OR gates. 10

- b) Implement 3 bit asynchronous up counter and also sketch the timing diagram. 10

Q6 Solve the following- 20

- Explain working of 8:1 Multiplexer.
- Working of S-R flip flop (with its internal circuit diagram and truth table).
- Explain working of Constant Current source.
- Write VHDL program for full subtractor.


(3 Hours)

[Marks: 80]


- N.B.: 1) Question No. 1 is compulsory.
2) Answer any three out of remaining questions.
3) Assume suitable data if necessary.
4) Figures to the right indicate full marks.

1. (a) Translate the given infix expression in to equivalent postfix expression. (3)
$$(a + b * c - d) / (e * f)$$

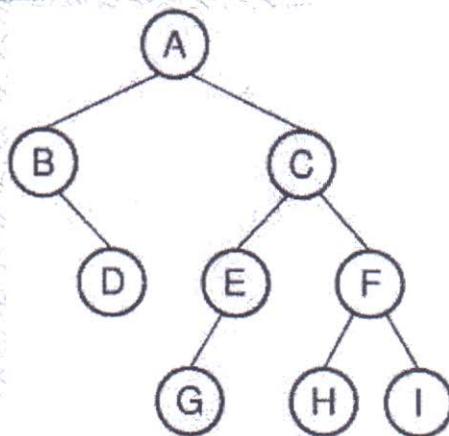(b) Explain linear and non linear data structures. (3)
(c) What is depth, height and degree of Binary tree. (3)
(d) What are the different ways to represent a graph? (2)
(e) What is linked list? Explain types of linked list. (3)
(f) What is recursion? State its advantages and disadvantages. (3)
(g) Explain asymptotic notations. (3)
2. (a) Write an algorithm for implementing queue using array. (10)
(b) Write an algorithm for merge sort and comment on its complexity. (10)
3. (a) Explain BFS and DFS algorithm with examples. (10)
(b) Traverse the following binary tree into preorder, inorder, postorder by giving its algorithm. (10)



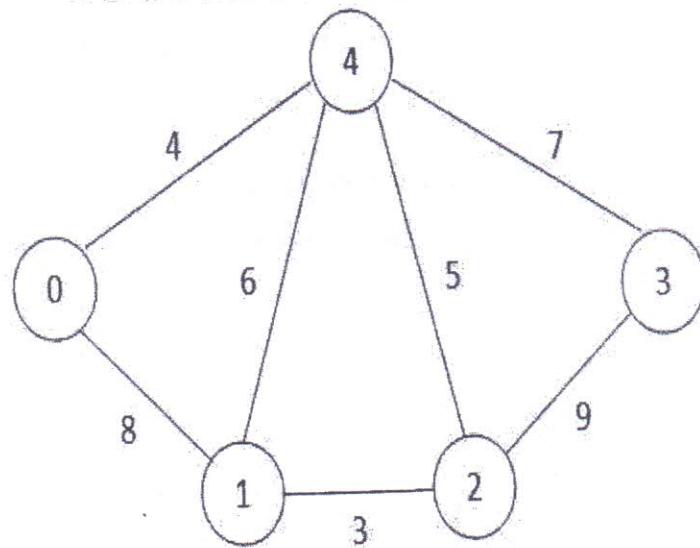4. (a) What is Doubly Linked List? Write an algorithm to implement following operations on Doubly linked List.
 (1)Insertion(All cases)
 (2)Traversal(Forward and Backward) 10
- (b) What is collision? What are the methods to resolve collision? Explain Linear probing with an example. 10
5. (a) What is Binary search tree. Construct Binary search tree for following elements:
13, 3, 4, 12, 14, 10, 5, 1, 8, 2, 7, 9, 11, 6, 18 10
- (b) Explain Heap sort using an example. Write algorithm for it and comment on its complexity. 10
6. (a) Write an algorithm for implementing stack using array. 10
- (b) What is Minimum Spanning Tree? Draw the MST using kruskal's and prim's algorithm and find out the cost with all intermediate steps. 10



- III .

Duration: 3 Hours

Marks: 80

- N.B (1) Question No. 1 is compulsory
 (2) Out of remaining questions attempt three
 (3) Figures to right indicate full marks.

Q1) Solve any four

20 (5*4)

- With the help of typical values ,state various RF bands along with their Applications.
- State Friiss formula & hence determine the overall noise figure in a two Stage cascaded amplifier if each stage has a gain of 10 dB along with a noise figure of 3 dB. (1+4)
- Define Image frequency of AM receiver & hence calculate image frequency Of AM superheterodyne receiver with RF & IF frequencies of 600 KHz & 455 KHz respectively. (1+4)
- Compare PAM, PWM & PPM system.
- Define the following
 - Quantization noise
 - line coding process
 - inter symbol interference
 - Bit rate
 - Baud Rate
- Explain ground wave propagation in brief

Q2 a) Explain following in relation to radio receiver with suitable figure

- Selectivity
- sensitivity
- double spotting
- fidelity

(10)

b) Explain the principle of TDM with neat diagram. Also explain need of synchronization in TDM.

(10) 6+4

Q3 a) What are different sources of noise? Classify & explain various noises that affect Communications. (10)

Q4 a) Explain/define/clarify the following term

(10)

- Modulation index in AM
- Modulation index in FM
- Over modulation in AM
- Total power in AM
- Transmission bandwidth in AM & FM

b) State & explain classification of line codes with neat figure

(10)

Q5 a) Draw the ASK, PSK & FSK waveforms for digital data 11010101

Also compare all three techniques of modulation

(6+4) (10)

b) State and prove following properties of Fourier transforms

- Time scaling
- frequency shifting.

(10)

Also state significance of these properties in communication system

(8+2)

20 (5*4)

Q6 Write short notes on following: Any Four

- a) Need of modulation
- b) Ratio detector
- c) Sky wave propagation
- d) Quantization process
- e) FM Noise triangle
- f) Block diagram of analog communication system