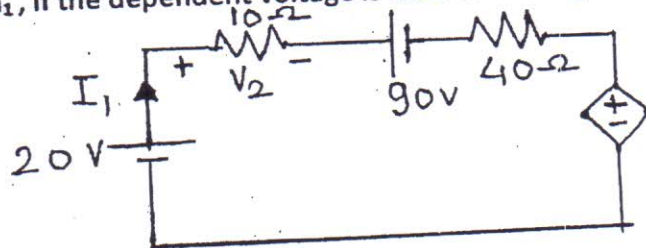


Note: 1. Question no.1 is compulsory.

2. Solve any three from the remaining questions.


a) Find  $I_1$ , if the dependent voltage is labelled as  $2V_2$



b) Draw oriented graph for the given incidence matrix

$$A = \begin{bmatrix} -1 & 1 & 0 & -1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

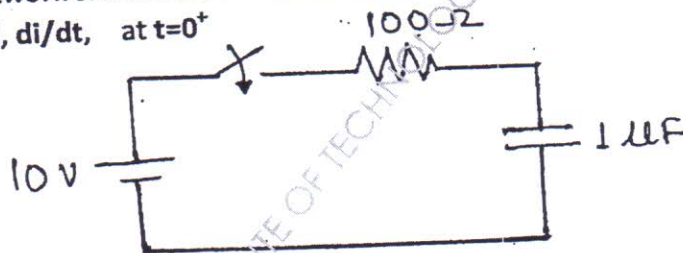c) In the network shown the switch is closed at  $t=0$ . With the capacitor uncharged, find value for  $i$ ,  $di/dt$ , at  $t=0^+$




d) Test whether the polynomial is Hurwitz

- 1)  $P(s) = s^6 + 3s^5 + 8s^4 + 15s^3 + 17s^2 + 12s + 4$
- 2)  $P(s) = s^8 + 5s^6 + 2s^4 + 3s^2 + 1$

Q2.

a) In the network shown the switch is changed from position 1 to 2 at  $t=0$ . Steady state condition having reached before switching, find value for  $i$ ,  $di/dt$ , &  $d^2i/dt^2$  at  $t=0^+$


(10)

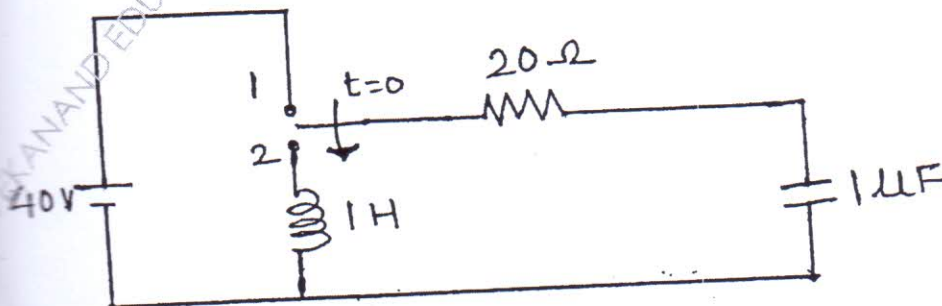

[TURN OVER

- b) Using the principle of network topology, find  $I$  in the fig.


(10)

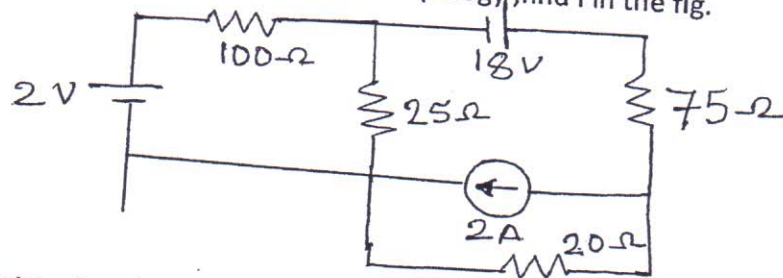

Q3.


- a) Determine thevenin's equivalent ckt for the shown network

(10)

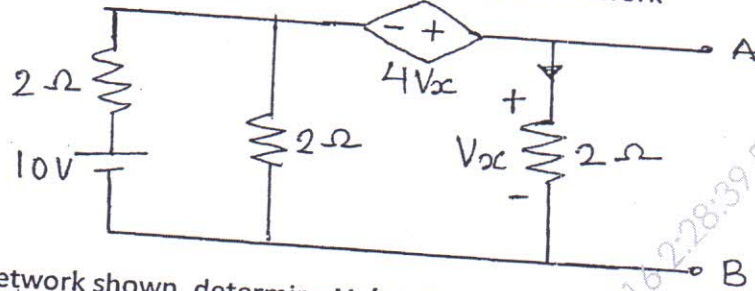

- b) For the network shown, determine  $V_2/V_1$  &  $V_2/I_1$


(10)

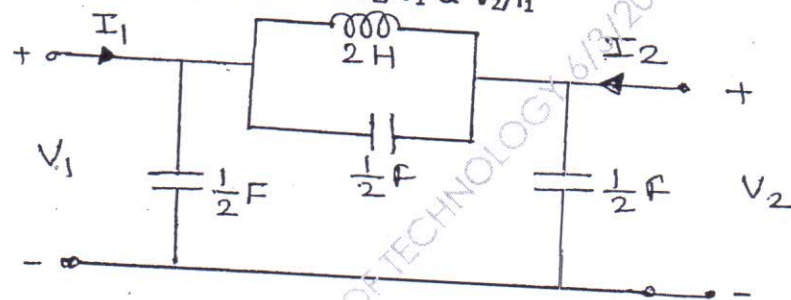

Q4.

- a) For the shown network, switch is closed at  $t=0$ . Find current  $i_1$  for  $t>0$

(10)

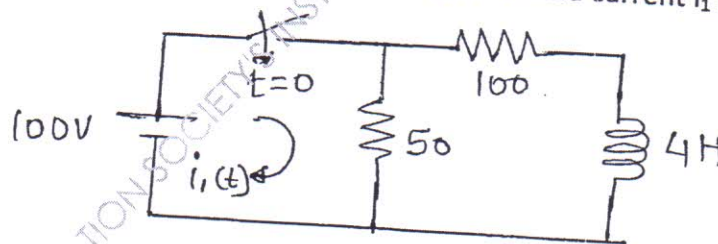


- b) Check the positive realness of the given functions

(10)

- 1)  $F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$
- 2)  $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$


a) For the shown network, find voltage  $V_{ab}$

(10)

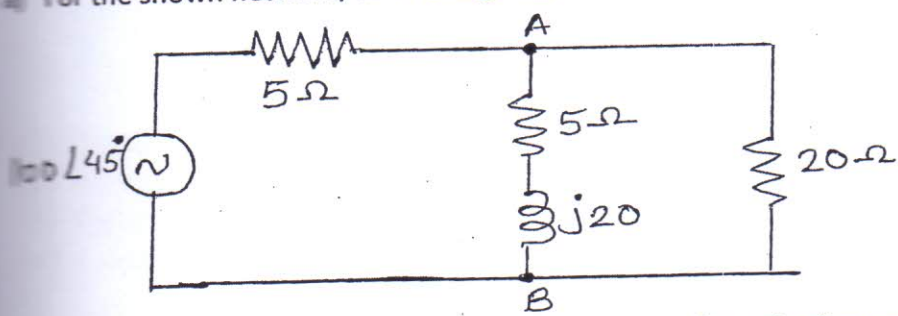

b) Determine Y parameters for the shown network. Also write Z-parameters from Y-parameters

(10)

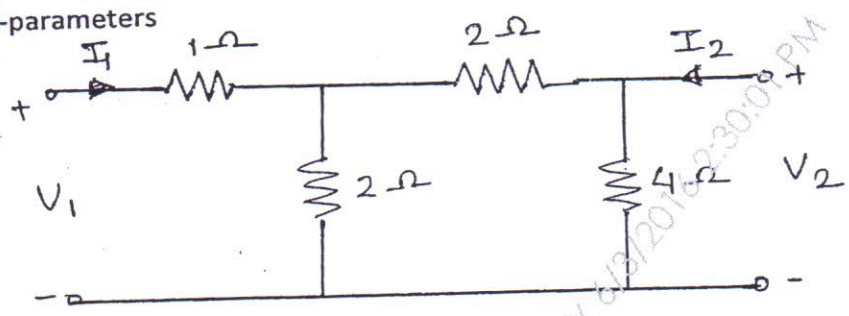


c) Synthesize the following RL function in Foster-I & Foster-II form

(10)

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$


d) Find  $I_1$  using mesh analysis

(5)

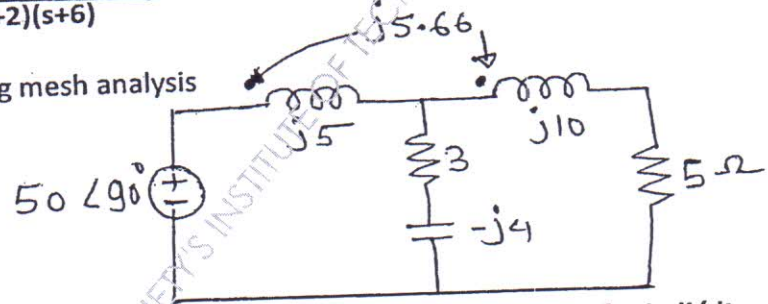

e) For the shown network, switch is closed at  $t=0$ . find value for  $i$ ,  $di/dt$

(5)

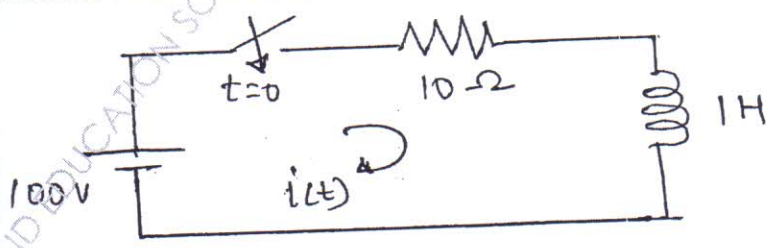

QP Code : 30705

(3 Hours)


[ Total Marks : 80

- (1) Question No. 1 is compulsory.
- (2) Attempt any three questions from remaining five questions.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.

Attempt any four questions from the following :-


20

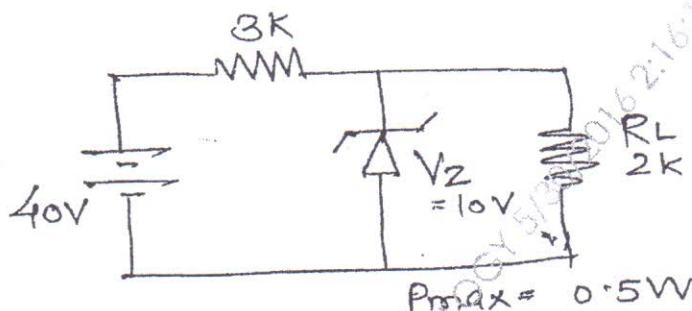- (a) Derive the stability factor  $S(I_{CO})$  for fixed bias circuit.
- (b) Calculate battery current  $I$ ,  $I_Z$  and  $I_L$  in circuit




- (c) How FET be employed as a voltage controlled resistor ?
- (d) Explain OP-AMP as summing amplifier averaging amplifier.
- (e) What are the ideal op-Amp characteristics?
- (f) Define and explain harmonic distortion'.

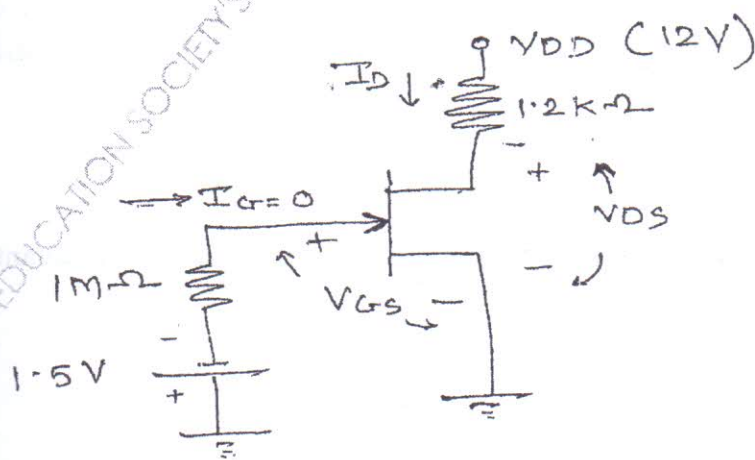- (g) Determine  $I_{DQ}$  and  $V_{DSQ}$  for following fixed bias configuration. It is given 10 that  $I_{DSS} = 12\text{mA}$  and  $V_p = -4\text{V}$




[TURN OVER

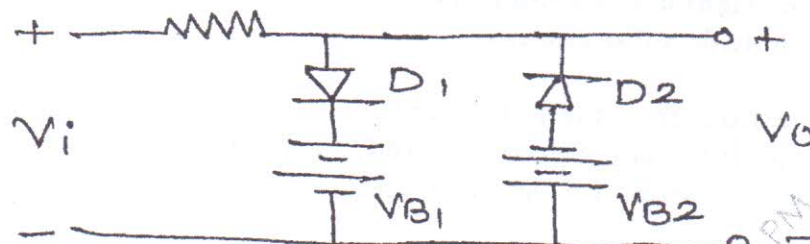- (b) Determine Output voltage. Assume,  $V_{B1} = 8\text{ V}$ ,  $V_{B2} = 6\text{ V}$  and input to be sine wave of 20V peak.



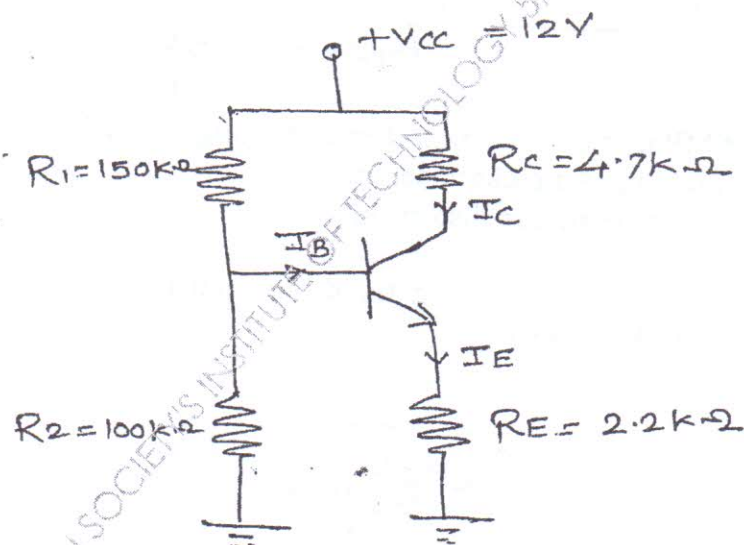- (c) Explain Low pass filter.
3. (a) For the circuit shown find the operating point co-ordinates. Given that  $\beta = 50$ ,  $V_{BE} = 0.7\text{ V}$




- (b) Derive equation for three op Amp Instrumentation amplifier. Give advantages and application of Instrumentation amplifier.

[TURN OVER

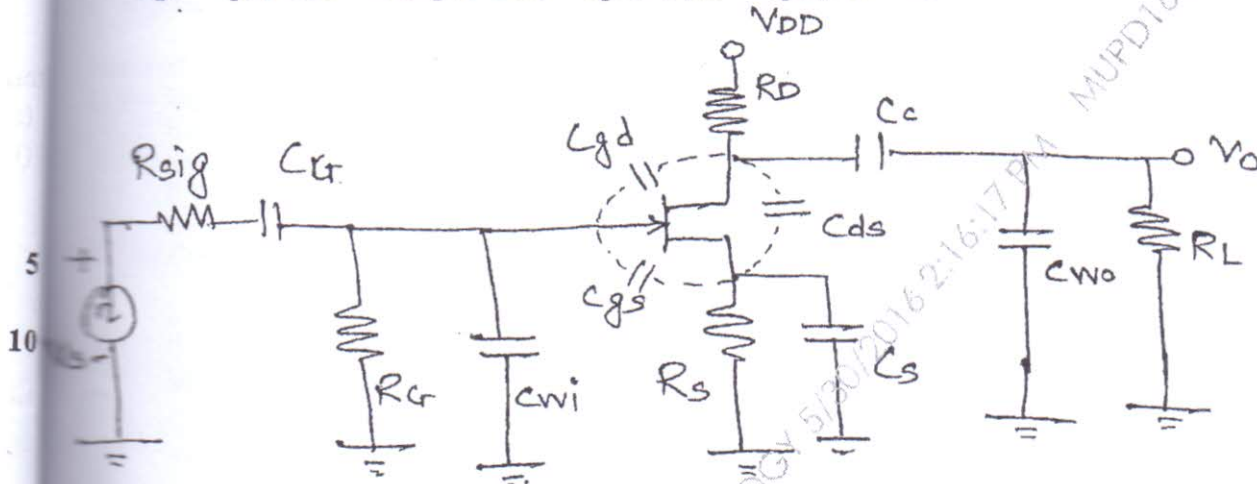(a) Determine the higher cut off frequencies for the given circuit diagram. 10

Given  $C_G = 0.01 \mu F$ ,  $C_C = 0.5 \mu F$ ,  $C_S = 2 \mu F$ ,  $R_{SIG} = 10K$ ,  $R_G = 1M$ ,  $R_D = 4.7K$ ,  $R_S = 1K$ ,  $R_L = 2.2K$ ,  $I_{DSS} = 8mA$ ,  $V_p = -4V$ ,  $r_d = \infty$ ,  $V_{DD} = 20V$ ,  $C_{gd} = 2pF$ ,  $C_{gs} = 4pF$ ,  $C_{ds} = 0.5 pF$ ,  $C_{wi} = 5pF$ ,  $C_{Wo} = 6pF$ ,  $A_v = -3$



(b) Write note on 'Transistor as Switch'. 10

(c) Explain with a neat diagram a transformer coupled audio power amplifier. 10

(d) Draw and explain Wien bridge oscillator. 5

(e) What do you understand by thermal runaway? 5

(f) Draw and explain a series voltage regulator. 10

(g) Draw the circuits for integrator and differentiator. Derive the necessary equation. Draw the frequency response of these circuits. 10

QP Code : 30560

(3 Hours)

[Total Marks : 80]

Question No. 1 is compulsory.

- (1) Attempt any THREE questions from remaining.
- (2) Figures to the right indicate full marks.
- (3) Assume suitable data if necessary.

1. Answer the following:-

[20]

- (a) State and prove De Morgan's theorems.
- (b) Implement 4:1 MUX using logic gates.
- (c) Explain the difference between combinational and sequential circuits.
- (d) Simplify the following expression using K Map.  
 $F = \sum (0, 2, 5, 7, 8, 10, 13, 15)$

2. (a) Convert :-

[10]

- i.  $(1010.101)_2$  to Decimal.
- ii.  $(1085)_{10}$  to Octal.
- iii.  $(1011)_2$  to Gray.
- iv.  $(34FB)_{16}$  to Binary.
- v.  $(177.1)_8$  to Binary.

(b) Perform: -

[05]

- i. Add  $(9BDE)_{16}$  and  $(ABCD)_{16}$
- ii. Divide 110110 by 101

(c) Compare demultiplexer and decoder.

[05]

3. (a) Prove the following using Boolean algebra and draw the logic circuit.

[10]

- i.  $(A+B)(A+\bar{B}) = A$
- ii.  $AB + \bar{A}C = AB + \bar{A}C + BC$

(b) Convert JK flip-flop to T flip-flop and D flip-flop.

[10]

4. (a) Design 4 bit Binary to Gray code converter.

[10]

(b) Implement full adder using logic gates.

[10]

5. (a) Design a MOD 3 synchronous counter using JK flip flops.

[10]

(b) What is Shift register? Explain the working of 4 bit bidirectional shift register.

[10]

6. Write note on: - (any Four)

[20]

(a) PAL and PLA, (b) ALU, (c) Priority Encoder, (d) ECL Family,

(e) Basic dynamic RAM Cell.

\*\*\*\*\*

FW-Con. 9414-16.

(3 Hours)

[ Total Marks : 80 ]

1. (1) Question No.1 is compulsory.  
 (2) Answer any **three** out of remaining **five** questions.  
 (3) Assume suitable data whenever required and state the assumptions.

Solve any **four** from the following

20

- What do you mean by calibration? What is need of calibration?
- Explain the principle of radiation type pyrometer.
- Define transducer and state its classification.
- Explain ultrasonic liquid level measurement.
- Define metrology and write its significance.

- Explain static and dynamic characteristics of an instrument 10
- Compare RTD, thermister and thermocouple. 10

- Explain use of potentiometer for displacement measurement 10
- The output of a LVDT is connected to 5V voltmeter through an amplifier whose amplification factor is 250. An output of 2 mV appears across the terminals of LVDT when core moves through a distance of 0.5mm. Calculate sensitivity of the LVDT and that of the whole setup. The millivoltmeter scale has 100 divisions. The scale can read of 1/5 of division. Calculate the resolution of the instrument in mm. 10

- Draw and explain schematic block diagram of hair hygrometer 10
- A platinum thermometer has a resistance of  $100\Omega$  at  $25^\circ\text{C}$ . 10
  - Find its resistance at  $65^\circ\text{C}$ , if the platinum has a resistance temperature coefficient of  $0.00392/^\circ\text{C}$ .
  - If the thermometer has a resistance of  $150\Omega$ , calculate the temperature.

- Explain Air purge type level gauge with advantages and disadvantages. 10
- Define error and explain types of error. 10

- Write short notes on following topic. (Any two) 20
  - Optical pyrometer
  - Cold junction compensation
  - Limits and fits