

(3 Hours)


[ Total Marks : 80 ]

- N.B. :**
- (1) Question No. 1 is Compulsory.
  - (2) Attempt **any three** questions from remaining **five** questions.
  - (3) All questions carry **equal** marks.


**I. Attempt any five :**

20

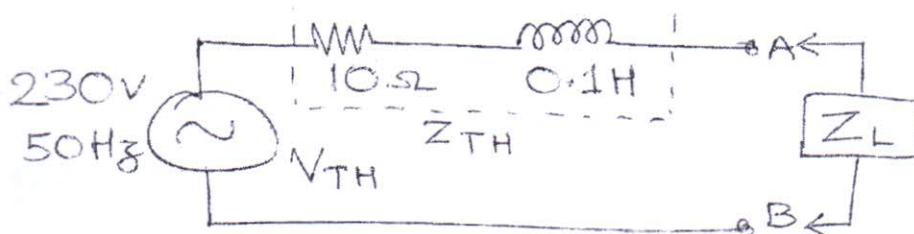
- (a) Determine value of  $Z_L$  for maximum power transfer and calculate max. Power.



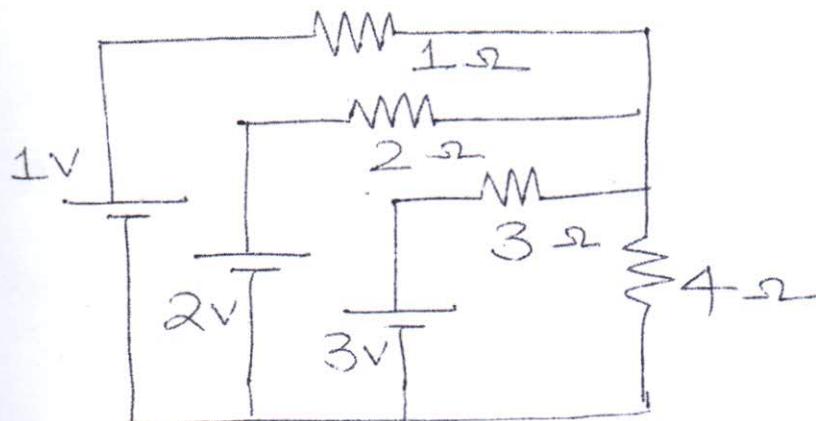- (b) Find  $I_{4\Omega}$  using Nodal analysis.



- (c) Obtain dual of given network

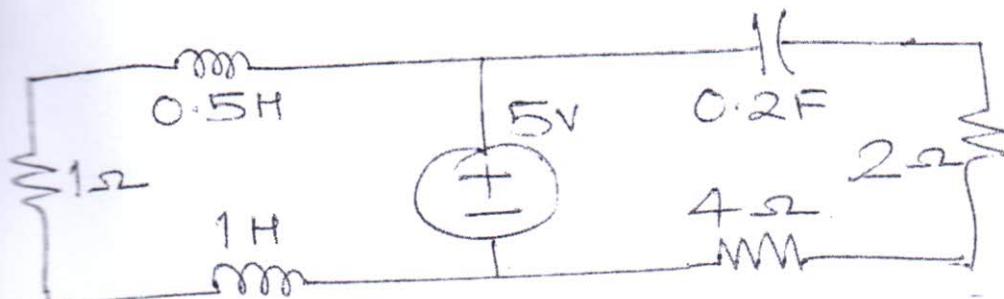

[TURN OVER]

2

- (d) If  $Z_{11} = 5\Omega$ ,  $Z_{22} = 7\Omega$ ,  $Z_{12} = Z_{21} = 3\Omega$  for a two part network, find ABCD parameters.

- (e) Find the current through a capacitor of value  $1/2 \text{ F}$  given that voltage across capacitor is


$$V_C(s) = \frac{1}{s^2 + 1}$$

- (f) Test whether following polynomial is Hurwitz.

$$P(s) = s^5 + 2s^3 + s$$


2. (a) Find  $V_x$  using superposition theorem.

10

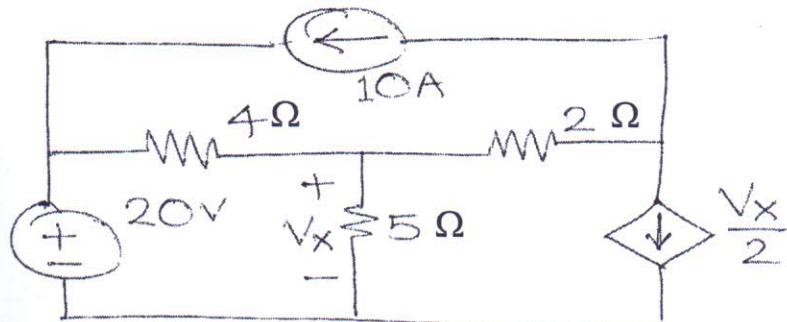


2. (b) Find voltage across  $5\Omega$  resistor.

10

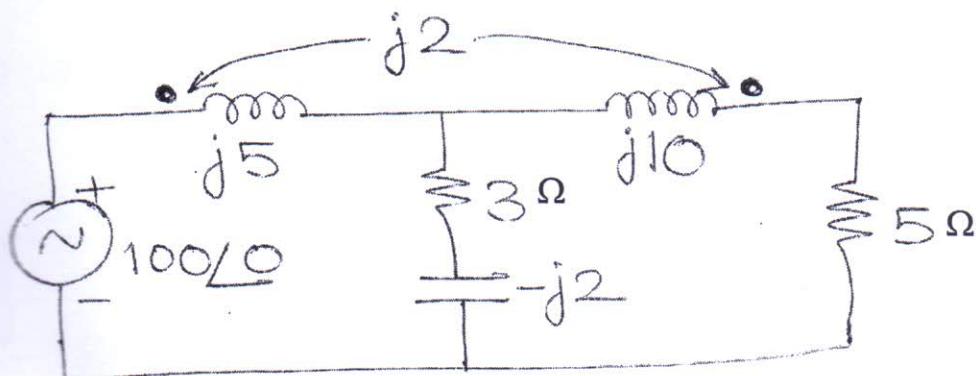


[TURN OVER]

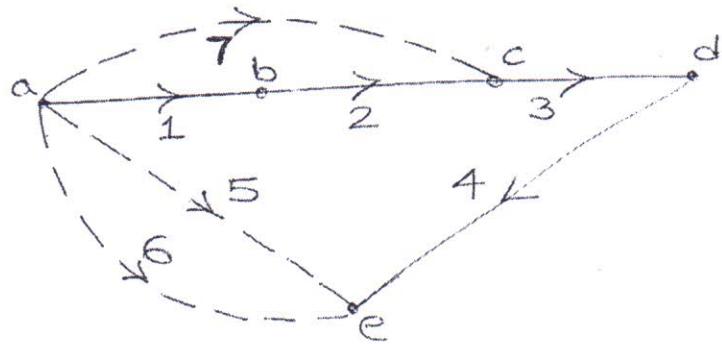3. (a) For given tree, find 10  
 (i) Incidence Matrix (ii) f-cutset matrix




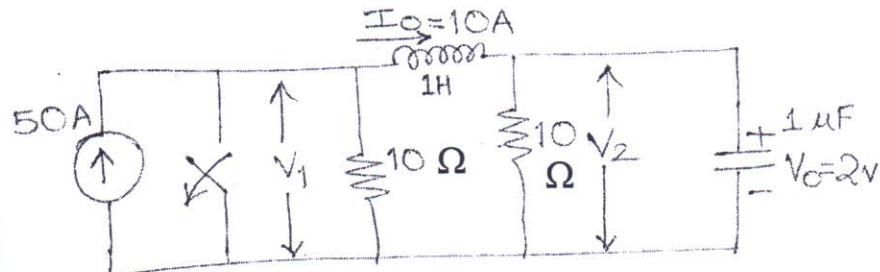- (b) For the network given below, switch is opened at  $t = 0$  with initial conditions 10  
 shown. Find the values of

$$V_1, V_2, \frac{dv_1}{dt}, \frac{dv_2}{dt} \text{ at time } t = 0^+$$



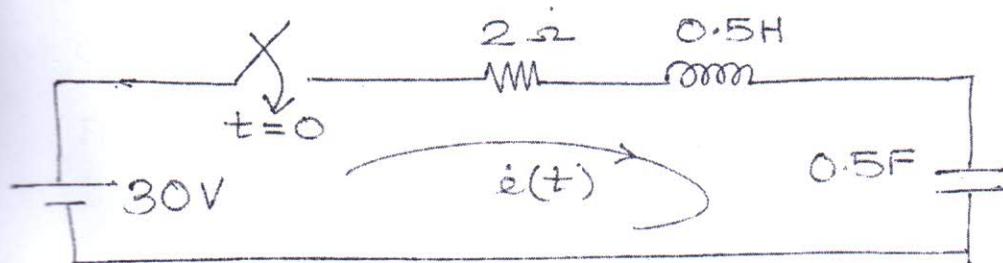4. (a) Obtain  $i(t)$  for the network shown. Use time domain approach. 10




[TURN OVER]

QP Code : 551002

4


- (b) Determine
- $i_1(t)$
- and
- $i_2(t)$

10

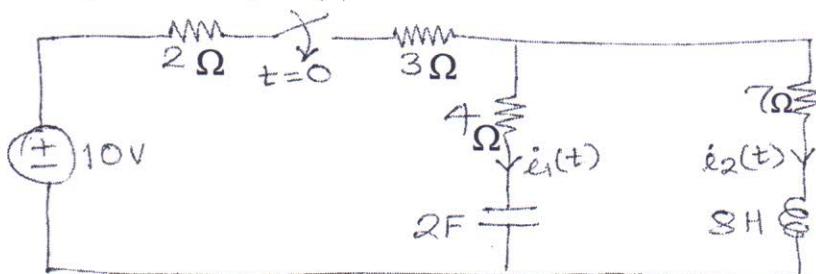


5. (a) Find ABCD parameter

10

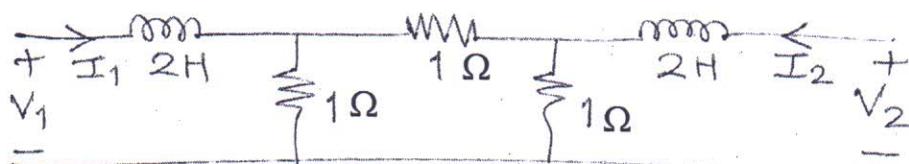

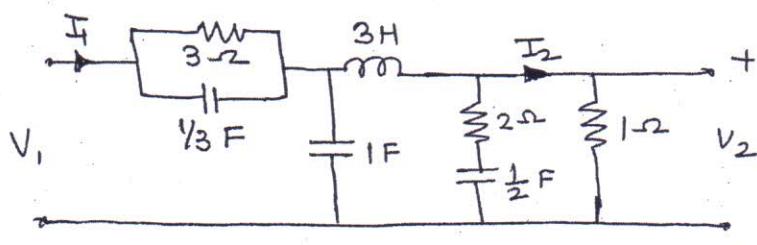- (b) Determine
- $\frac{I_2}{I_1}$
- for network



6. (a) Check for positive real function.

$$F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

10

$$(b) Y(S) = \frac{4(s^2 + 4)(s^2 + 25)}{s(s^2 + 16)}$$

10

Find Foster II and Cauer I forms.

Q.P. Code : 550902




(3 Hours)

[ Total Marks : 80 ]

N.B. : (1) Question No. 1 is compulsory.

- (2) Attempt any THREE from remaining five questions.  
 (3) All questions carry equal marks.  
 (4) Assume suitable data wherever necessary.

1. Answer any four questions from the following :-

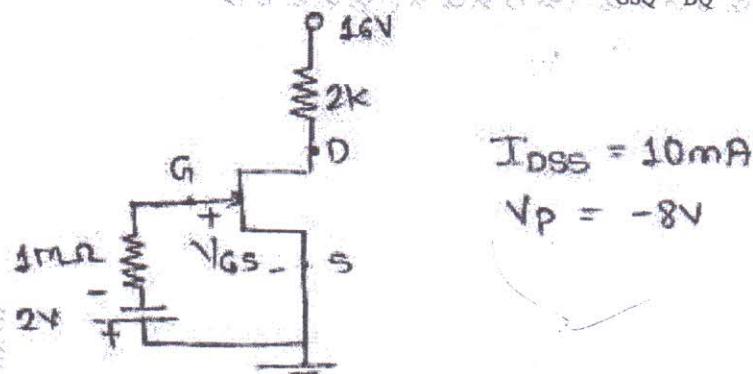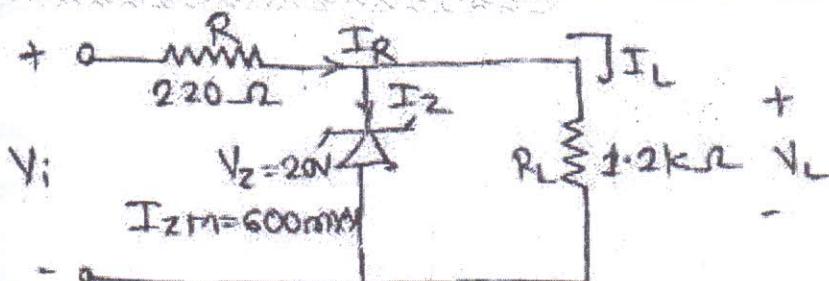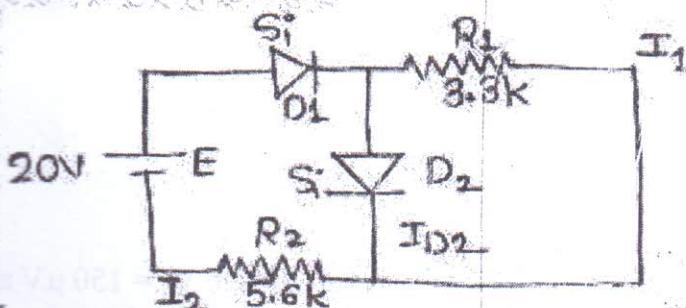
a) Determine the following for fixed bias configuration  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DS}$ ,  $V_G$ ,  $V_S$ .b) Determine range of  $V_i$  that will maintain zener diode in ON state.c) Determine  $I_1$ ,  $I_2$  and  $I_{D2}$  for network given below.

[ TURN OVER ]

Q.P. Code : 550902

2

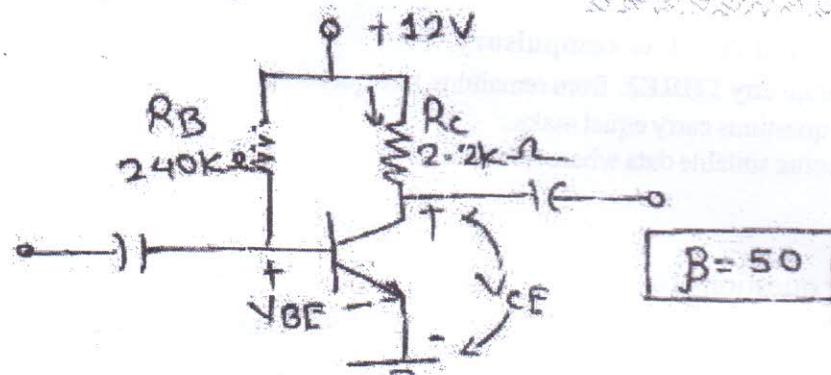
d) Find  $I_{CQ}$  and  $V_{CEQ}$  for given network.



e) Define rectifier and explain any one type of full wave rectification.

2. a) Determine output voltage with silicon diode with  $V_T = 0.7V$ .

8

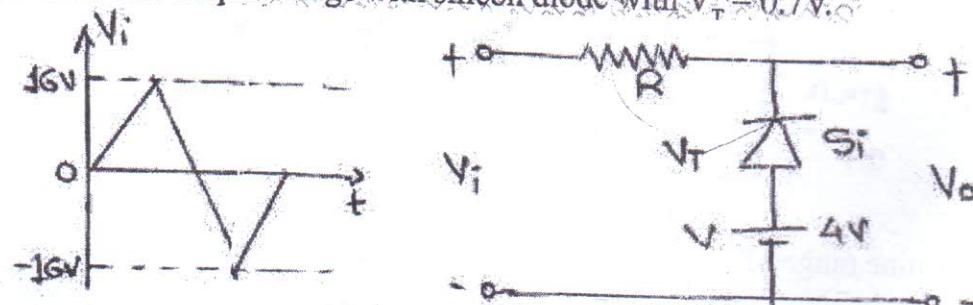

b) Explain four types of controlled sources of op amp.


8

c) Op amp having  $SR = 2V/\mu S$ . What is maximum close loop gain that can be used when input signal varies by  $0.5V$  in  $10\mu s$ .

4

3. a) Determine  $I_1$ ,  $V_1$ ,  $V_2$  and  $V_o$  for the series dc configuration.

5

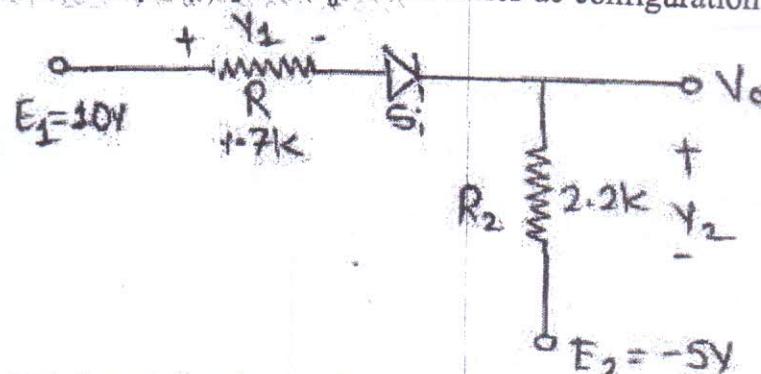

b) Determine output voltage of an op amp for input voltage  $V_{i1} = 150 \mu V$  and  $V_{i2} = 140 \mu V$ . The amplifier has a differential gain of  $A_d = 4000$  and value of CMRR is  $10^6$

5


[ TURN OVER]

Q.P. Code : 550902


3

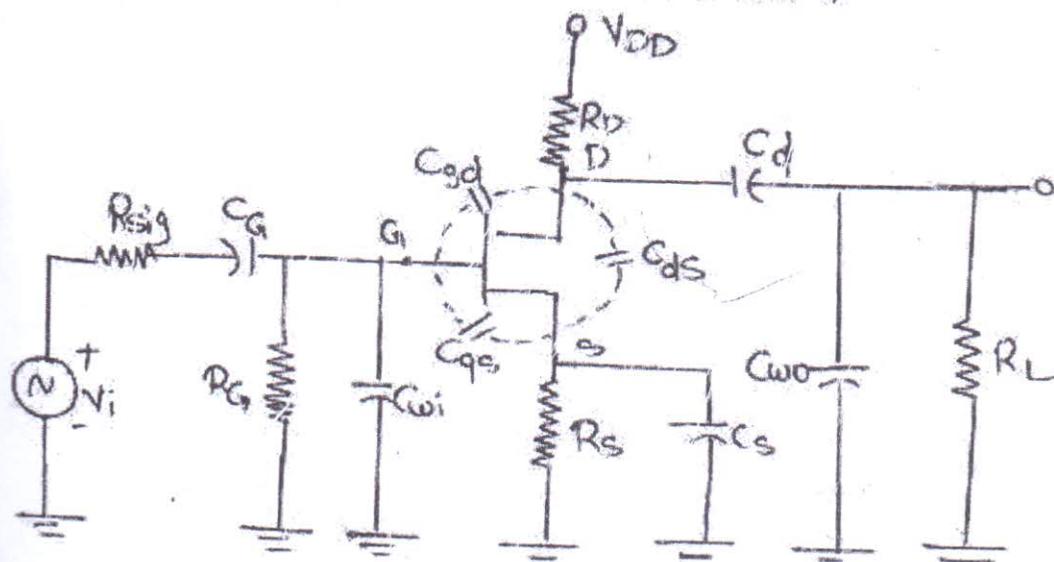- c) List the biasing techniques of FET And explain any two techniques in detail. 10
4. a) Explain integrator and its frequency response. Explain how practical integrator overcomes disadvantages of basic integrator. 10  
 b) Define oscillator. State condition of oscillation. Explain RC phase oscillator. 10
5. a) Determine high frequency and low frequency response of network shown Below 10

$C_G = 0.01 \mu F$ ,  $C_C = 0.5 \mu F$ ,  $C_S = 2 \mu F$ ,  $R_{SIG} = 10K\Omega$ ,  $R_G = 1M\Omega$   
 $R_D = 4.7K\Omega$ ,  $R_S = 1K\Omega$ ,  $R_L = 2.2K\Omega$ ,  $I_{DSS} = 8$ ,  $V_P = -4V$ ,  $r_d = \infty \Omega$ ,  $V_{DD} = 20V$   
 $A_V = -3$ ,  $C_{GD} = 2pF$ ,  $C_{GS} = 4pF$ ,  $C_{DS} = 0.5pF$ ,  $C_{WI} = 5pF$ ,  $C_{WO} = 6pF$



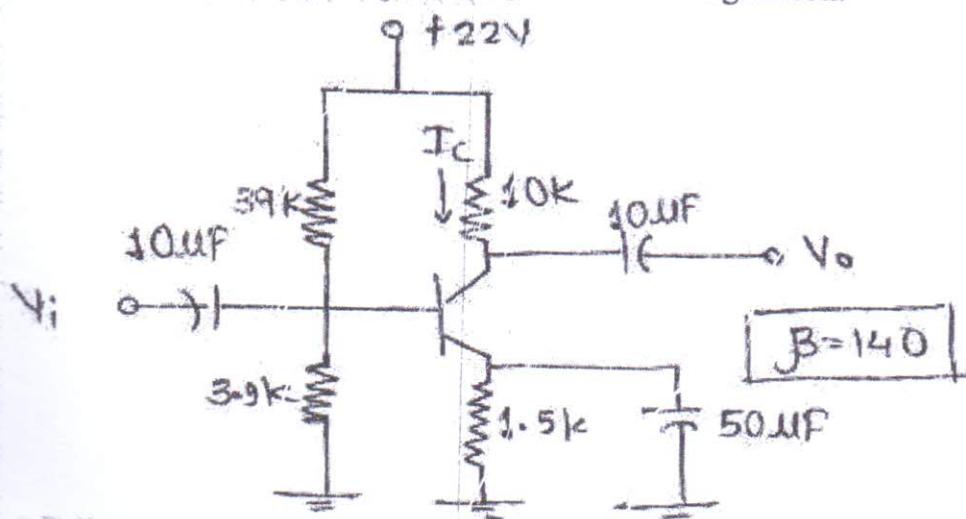- b) Determine  $V_{CE}$  and current  $I_C$  for voltage divider configuration. 10




[ TURN OVER]

Q.P. Code : 550902

4

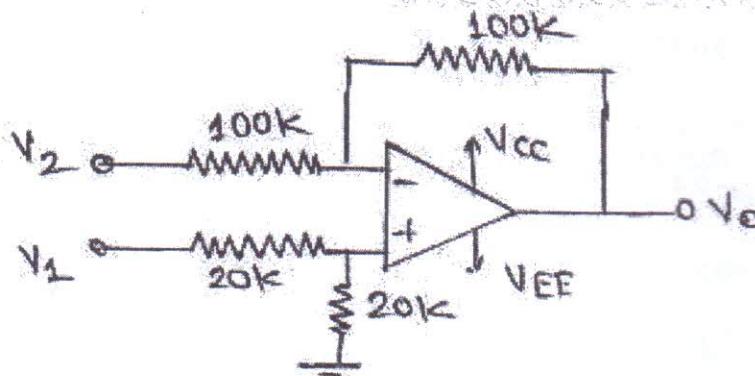6. a) Draw and explain series voltage regulator.  
 b) Write a note on Schmitt trigger.  
 c) Bias compensation techniques.  
 d) Derive expression for output voltage and hence determine output voltage when  $V_1 = V_2 = 1V$ .



Q. P. Code : 550602

(3 Hours)

(Total Marks : 80)

- N.B.**
- (1) Question no 1 is compulsory.
  - (2) Attempt any three questions from the remaining questions
  - (3) Figures to the right indicate full marks.
  - (3) Assume suitable data wherever necessary.

1. Answer the following (any four)
  - (a) Convert: (i)  $(24.165)_{10}$  into Hexadecimal, binary & octal number. 20
  - (b) Realize AND & EX-OR gate using NOR gate.
  - (c) Convert the following equation in standard SOP form.  

$$Y = \bar{A}B + AC + BC$$
  - (d) Perform following operations.
    - (i)  $(110011)_2 - (101100)_2$
    - (ii)  $(101100)_2 - (110011)_2$
  - (e) Convert the binary number  $(11011011.1102)_2$  into decimal, Hexadecimal & octal form.
2. (a) Design 32:1 Multiplexer using 8:1 Multiplexer & suitable gates. 10  
 (b) Obtain the minimal expression using Quine Mc Cluskey method.  
 $f(A,B,C,D) = \sum m(1,4,5,12,13,14) + d(2,7)$  10
3. (a) Implement the following logic using 4:16 decoder.  
 $F_1 = \sum m(1,2,4,8,11,12,13)$  10  
 $F_2 = \sum m(10,12,8,13,14)$   
 $F_3 = \sum m(2,3,4,11)$   
 $F_4 = \sum m(2,4,6,8)$   
 (b) Design mode 7 synchronous counter using J.K. flip flop. 10
4. (a) Design 4 bit BCD adder using IC 7483. 10  
 (b) Design & implement 4 bit binary to gray converter. 10
5. (a) Explain the operating of 4 bit bidirectional shift register with neat diagram. 10  
 (b) Draw & explain master slave JK flip flop. Describe how it eliminates race around condition. 10
6. Write a short notes on:- (any four)
  - (1) Explain CMOS inverter.
  - (2) Compare PAL & PLA.
  - (3) Compare T & D Flip Flop.
  - (4) Explain Johnson counter.
  - (5) State & prove De Morgan's theorem20

\*\*\*\*\*

**Q.P. Code : 550800****(3 Hours )****[ Total Marks : 80 ]**

- N.B. :** (1) Question No.1 is compulsory.
- (2) Attempt any three out of remaining.
- (3) Figures indicate to the full marks.
- (4) Assume suitable data if necessary.

1. Answer the following. 20
  - a) Classify transducers with suitable example.
  - b) Draw and explain Flapper-Nozzle system.
  - c) What is the principle of working of capacitive transducers? How can we use them for level measurement?
  - d) Find seebeck voltage for a thermocouple with proportionality constant of  $40\mu\text{V}/^\circ\text{C}$  If the junction temperature are  $40^\circ\text{C}$  and  $80^\circ\text{C}$ .
  - e) A thermistor has a resistance temperature coefficient of  $-5\%$  over a temperature range of  $25^\circ\text{C}$  to  $50^\circ\text{C}$ . If the resistance of the thermistor is 100 ohms at  $25^\circ\text{C}$ , what is the resistance at  $35^\circ\text{C}$ ?
2. a) Draw and explain working of LVDT. What causes residual voltage to occur? 10
  - b) A linear resistance potentiometer is 50mm long and is uniformly wound with a wire having resistance of  $10,000\ \Omega$  under normal condition. The slider is at the center of the pot. Find the linear displacement when the resistance of pot is measured by Wheatstone's bridge for two cases  
(i)  $3850\ \Omega$  (ii)  $7560\ \Omega$ . Are the two displacements in the same direction?
3. a) Explain any five static characteristics of transducer with suitable examples. 10
  - b) What is the need of lead wire compensation? How it is to be done in RTD? 10  
What is self heating effect in RTD?
4. a) For a certain thermistor  $\beta = 3140\ \text{K}$  and at  $27^\circ\text{C}$  is known to be  $1050\ \Omega$ . 10  
The thermistor is used for temperature measurement and the resistance measured is as  $2330\ \Omega$ . Find the measured temperature.
- b) Draw set up and explain working of air purge method of level measurement. 10
5. a) Explain in detail radioactive type level detector. 10

**[ TURN OVER]**

**Q.P. Code : 550800**

2

- b) A capacitive transducer uses two quartz diaphragm of area  $750 \text{ mm}^2$  separated by a distance of 3.5 mm. A pressure of  $900 \text{ KN/m}^2$  when applied to top diaphragm produces a deflection of 0.6 mm. The capacitance is  $370\text{pF}$  when no pressure is applied to the diaphragm. Find the value of capacitance after the application of pressure  $900 \text{ KN/m}^2$ . **10**
6. Write short notes (any two) :- **20**
- Optical pyrometer
  - Rotary encoder
  - Metrology & need of inspection