

Duration: 03 Hours

Total Marks: 80 Marks


Instruction to candidate:-

1. Question 1 is compulsory.
2. Attempt any three from remaining five questions.
3. All questions carry equal marks.
4. Assume suitable data wherever necessary.


Q1. Attempt any four

[20 Marks]

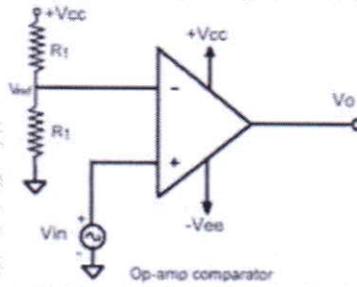
- Q1.a Define slew rate. For an op-amp having a slew rate of  $SR = 2.4 \text{ V}/\mu\text{s}$ , what is the time taken for output to change from  $-15 \text{ V}$  to  $+15 \text{ V}$ .
- Q1.b Explain operation of following comparator circuit. Consider input as sine wave of  $10 \text{ V}$  and supply voltage of  $15 \text{ V}$ .



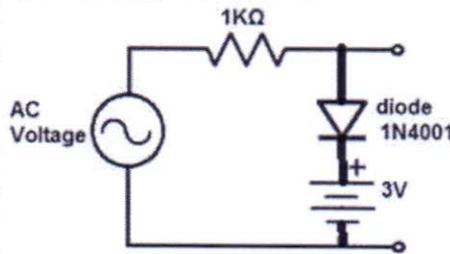- Q1.c With example, explain operation of transistor as a switch.
- Q1.d Gate current is effectively zero for an FET, justify.
- Q1.e Explain bridge rectifier.
- Q2.a Determine output voltage. Assume, input to be sine wave of  $5 \text{ V}$  peak. Draw waveform considering ideal and practical diodes. [10 Marks]



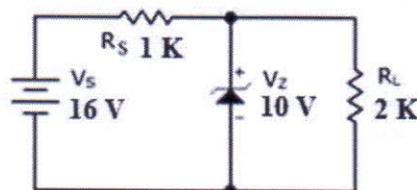Q2.b For the Zener diode network, determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ . [10 Marks]



Q3.a BJT transistor with voltage divider bias circuit has following values,  $V_{CC} = 20\text{ V}$ ,  $R_1 = 40\text{ K}$ ,  $R_2 = 4\text{ K}$ ,  $R_C = 10\text{ K}$ ,  $R_E = 1.2\text{ K}$ ,  $\beta = 140$ . Determine operating point and  $V_{BC}$ . [8 Marks]

Q3.b Determine operating point and  $V_{DS}$  for an FET self biasing circuit with  $V_{DD} = 18\text{ V}$ ,  $R_D = 1.5\text{ K}$ ,  $R_S = 750$ ,  $R_G = 1\text{ M}$ ,  $I_{DSS} = 10\text{ mA}$  and  $V_P = -4\text{ V}$ . [8 Marks]

Q3.c Explain E-MOSFET. [4 Marks]


Q4.a Derive the expression of stability factor for voltage biasing circuit. [10 Marks]

Q4.b Draw and explain series voltage regulator. [10 Marks]


Q5.a Draw the circuits for integrator and differentiator. Derive the necessary equation. Draw the frequency response of these circuits. [10 Marks]

Q5.b Explain three OpAmp instrumentation amplifier. [10 Marks]

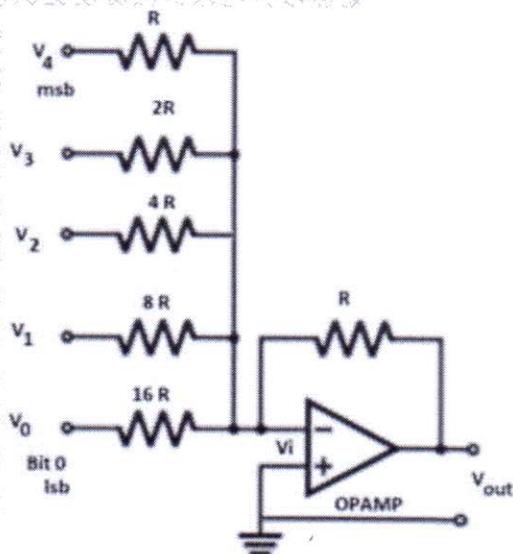
Q6.a Derive output equation and calculate output voltage if,  $V_0 = V_2 = V_4 = 5\text{ V}$  and  $V_1 = V_3 = 0\text{ V}$ . [5 Marks]



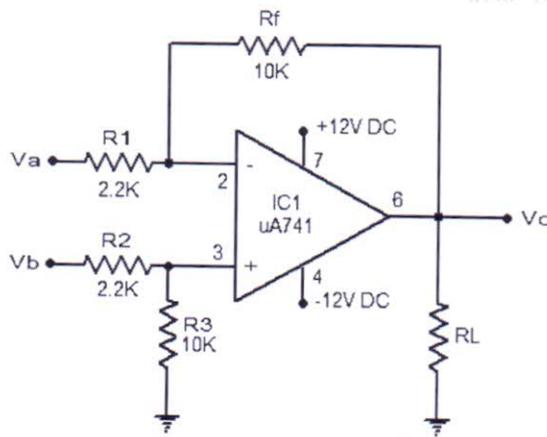Q6.b Derive output equation and calculate output voltage if,  $V_a = V_b = 700 \text{ mV}$ ,  $R_1 = R_2 = 2.2 \text{ K}$ ,  $R_3 = R_f = 10 \text{ K}$ . [5 Marks]



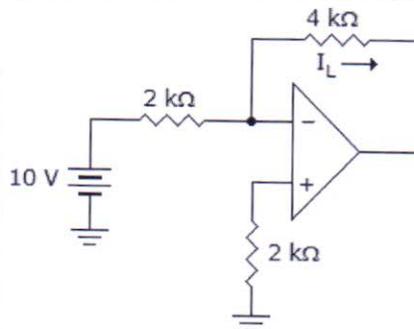Q6.c Identify the circuit diagram. Calculate  $I_L$  for this circuit. [5 Marks]



Q6.d Explain RC phase shift oscillator using OpAmp. [5 Marks]