

(3 Hours)

Total Marks: 80

Note:-

- 1) Question number 1 is compulsory.
- 2) Attempt any three questions from the remaining five questions.
- 3) Figures to the right indicates full marks

- Q.1**
- a) Evaluate Laplace transform of $t e^{3t} \sin 4t$ 05
 - b) Find half range fourier sine series for x^2 in $(0, \pi)$ 05
 - c) Find the directional derivative of $4xz^2 + x^2yz$ at $(1, -2, -1)$ in the direction of $2\bar{i} - \bar{j} - 2\bar{k}$ 05
 - d) Find k such that $\frac{1}{2} \log(x^2 + y^2) + i \tan^{-1} \left(\frac{kx}{y} \right)$ is analytic 05
- Q.2**
- a) Show that the function is Harmonic and find it's conjugate $u = e^{2x}(x \cos 2y - y \sin 2y)$ 06
 - b) Evaluate $L^{-1} \left[\frac{s^2}{(s^2+9)(s^2+4)} \right]$, using convolution theorem 06
 - c) Verify Green's theorem in the plane for $\int_C (xy + y^2)dx + x^2dy$, where C is the region bounded by the curves $y = x$ and $y = x^2$ 08
- Q.3**
- a) Solve $(D^2 + 2D + 1)y = 3te^{-t}$, $y(0) = 4$, $y'(0) = 2$ by using Laplace transform. 06
 - b) Show that $\bar{F} = (4xy + 3x^2z)\bar{i} + (2x^2 - 2z)\bar{j} + (x^3 - 2y)\bar{k}$ is conservative. Find the work done in moving a particle from $A(1,0,1)$ to $B(2,1,1)$. 06
 - c) Find the Fourier series for the function $f(x) = \left(\frac{\pi-x}{2} \right)^2$ in the interval $0 \leq x \leq 2\pi$. Hence deduce $\frac{\pi^2}{6} = \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots$ 08
- Q.4**
- a) Obtain the Fourier Series of $x \cos x$ in $(-\pi, \pi)$ 06
 - b) Find the bilinear transformation which maps the points $z = i, -1, 1$ onto the points $w = 0, 1, \infty$ 06
 - c) Evaluate i. $L^{-1} \left[\tan^{-1} \left(\frac{a}{s} \right) \right]$ ii. $L^{-1} \left[\frac{e^{-\pi s}}{s^2 - 2s + 2} \right]$ 08
- Q.5**
- a) Evaluate $\int_0^\infty e^{-t} \left[t \int_0^t e^{-4u} \cos u \, du \right] dt$ 06
 - b) Show that under the transformation $w = \frac{z-i}{z+i}$, real axis in Z -plane is mapped onto the circle $|w| = 1$ 06
 - c) Find the Fourier expansion of $f(x) = x^2$ in $(0, a)$. Hence deduce that $\frac{\pi^2}{-3} = \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \frac{1}{4^2} \dots$ 08

- Q.6 a) Find the orthogonal trajectories of the family of curves $x^2 - y^2 + x = c$
- b) Find the Fourier cosine integral representation of the function
- $$f(x) = \begin{cases} 1 - x^2, & 0 \leq x \leq 1 \\ 0, & x > 1 \end{cases}$$
- Hence evaluate $\int_0^\infty \left(\frac{x \cos x - \sin x}{x^3} \right) \cos \frac{x}{2} dx$
- c) Evaluate by using Gauss Divergence theorem $\iint_S \vec{N} \cdot \vec{F} ds$, where $\vec{F} = 4x\vec{i} + 3y\vec{j} - 2z\vec{k}$. S is the surface bounded by $x=0, y=0, z=0$ and $2x + 2y + z = 4$.

[Time: Three Hours]

[Marks:80]

1. Question.No.1 is compulsory.
2. Attempt any three questions from remaining five questions.
3. Assume suitable data wherever necessary.

Attempt any five questions.

[20 Marks]

- a) Explain any one method of full wave rectification with the help of labelled diagram.
- b) How transistors can be used as switches?
- c) Plot the output waveform for the circuit shown below (Fig.1).

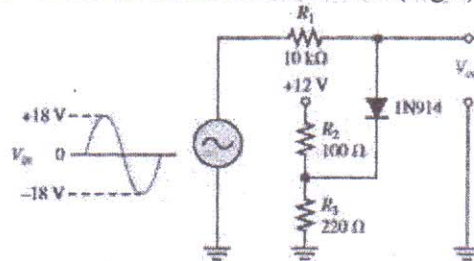


Fig.1

- d) Design an inverting amplifier whose gain is variable over the range $-4 \leq A \leq 0$ by means of a $10K\Omega$ pot.
- e) Define and explain harmonic distortion.
- f) Sketch the output waveform for the circuit of fig.2, if the input signal is a 5 V peak sine wave.

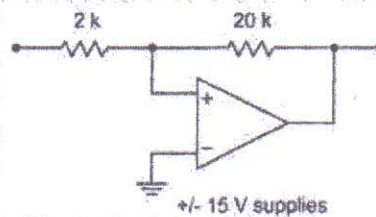


Fig.2

- a) Determine V_o and I_D for the series circuit of Fig. 3.

[6 Marks]

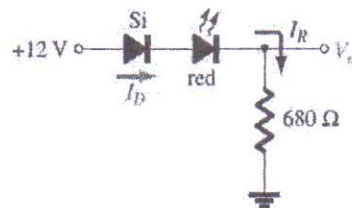


Fig. 3

- b) Derive the stability factor $S(I_{co})$ for emitter stabilized Bias circuit. Calculate $S(I_{co})$ for the same circuit if $R_B=510 K\Omega$, $R_C=2.4 K\Omega$, $R_E=1.5 K\Omega$, $V_{CC}=2.4 K\Omega$ and $\beta=100$.

[8 Marks]

- c) What are the characteristics of an ideal op-amp? Explain why open loop configurations are not used in linear applications.

[6 Marks]

- Q.3 a) Find I_c and V_{EC} for the pnp transistor

[6 Marks]

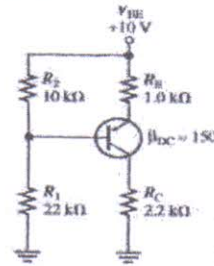


Fig.4

- b) Explain thermal runaway in case of the BJT. How we can do compensation for the same. [6 Marks]
 c) The transistor in Fig.5 has the following maximum ratings: $P_D(\text{max}) = 800 \text{ mW}$, $V_{CE}(\text{max}) = 15 \text{ V}$, and $I_C(\text{max}) = 100 \text{ mA}$. Determine the maximum value to which V_{CC} can be adjusted without exceeding a rating. Which rating would be exceeded first? [8 Marks]

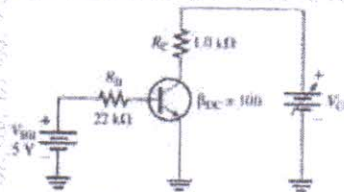


Fig.5

- Q.4 a) Explain the working of D MOSFET with neat diagrams. [8 Marks]
 b) Explain with a neat diagram a transformer coupled audio power amplifier. [6 Marks]
 c) Sketch the 3-input inverting averaging circuit and derive an equation for the output voltage. [6 Marks]
- Q.5 a) Write the design procedure for High pass filter with suitable example. [8 Marks]
 b) What are the conditions for stable oscillations? Draw the circuit of Wein Bridge oscillator and derive equations for frequency and gain. [6 Marks]
 c) What is the basic difference between a basic comparator and the Schmitt trigger. For an inverting Schmitt trigger if $R_1 = 180 \Omega$, $R_2 = 80 \text{ K}\Omega$, $V_{in} = 500 \text{ mV}_{pp}$ sine wave, and the saturation voltages are $\pm 15 \text{ V}$. Determine upper, lower threshold voltage and hysteresis voltage. [6 Marks]

Q6

- Draw and explain series voltage regulator. [6 Marks]
- Explain four types of controlled sources using opamp. [6 Marks]
- Derive the expression for the circuit shown below, Plot the waveforms for output voltage of the ideal op-amp shown in fig.6 for the triangular-wave input shown below. [8 Marks]

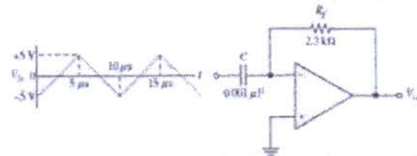


Fig.6

[Time: Three Hours]

[Marks:80]

- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three questions from remaining five questions.
 3. Assume suitable data wherever necessary.

20

Attempt any four :

- Explain absolute humidity and relative humidity.
 - What do you mean by calibration? What is the need of calibration?
 - Explain sensor characteristics i) Hysteresis and ii) Linearity.
 - What is base metal and rare metal thermocouples? State their advantages and disadvantages.
 - Explain liquid level measurement using float and LVDT with appropriate diagram.
- Explain different types of errors in measurements with their remedies. 10
 - Explain flapper nozzle system and comment on its application. 10
 - Explain radioactive type level detector in detail. 10
 - A capacitive transducer uses two quartz diaphragms of area 750 mm^2 separated by a distance of 3.5 mm . A pressure of 900 kN/m^2 when applied to the top diaphragm produces a deflection of 0.6 mm . The capacitance is 370 pF when no pressure is applied to the diaphragms. Find the value of capacitance after the application of a pressure of 900 kN/m^2 . 10
 - State different types of pyrometers. Explain with a neat sketch any one of them. 10
 - State and explain laws of intermediate temperature and intermediate metals of thermocouple. Write the significance of these laws. 10
 - Explain construction and working principle of LVDT. 10
 - A linear resistance potentiometer is 50 mm long and is uniformly wound with a wire having a resistance of $10 \text{ K} \Omega$. Under normal conditions, the slider is at the center of the potentiometer. Find the linear displacement when the resistance of the potentiometer as measured by a Wheatstone bridge for two cases is i) 3850Ω ii) 7560Ω . Are the two displacements in the same direction? If it is possible to measure a minimum value of 10Ω resistance with the above arrangement, find the resolution of the potentiometer in mm . 10
 - Write a short note on (Any two) :- 20

 - Hall Effect Transducer
 - Sound Pressure Level meter
 - Air purge type level gauge.
 - Lead wire compensation in RTD

(3 Hours)

[Total Marks: 80]

NOTE: (1) Question No. 1 is compulsory.

- (2) Attempt any **THREE** questions from remaining.
 (3) **Figures to the right indicate full marks.**
 (4) Assume suitable **data** if necessary.

1. Answer the following: -

[20]

- (a) Implement EX- OR logic gate using NAND gates.
 (b) Explain Fan-In and Fan-Out of digital ICs.
 (c) Explain the working of SR flip flop? What is meant by edge triggering?
 (d) Implement $f(ABC) = \sum m(1,2,5)$ using 4:1 MUX.

2. (a) Prove the following using Boolean algebra.

[10]

i) $(A + \bar{B} + AB)(A + \bar{B})(\bar{A}B) = 0$

ii) $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = AB + AC + BC$

(b) Perform:- i) $(24)_8 - (10)_8$ ii) $(64)_{16} + (33)_{16}$

[05]

(c) Convert:

[05]

i) $(9CD)_{16} = (?)_{10}$ ii) $(0.42)_{10} = (?)_2$

3. (a) Design a 4 bit BCD adder using IC 7483.

[10]

(b) Design two-bit magnitude Comparator using logic gates.

[10]

4. (a) Design 3 bit synchronous counter using JK flip- flop.

[10]

(b) Explain with a neat diagram working of SISO shift register.

Draw necessary timing diagram.

[10]

5. (a) What is FPGA? What are its salient features?

[05]

(b) What are the merits and demerits of TTL family?

[05]

(c) Design and implement a full subtractor circuit using 3: 8 Decoder.

[10]

6. Write note on: - (Any Four)

[20]

- (a) Hazards and Hazard elimination.
 (b) PAL and PLA.
 (c) Advantages of 2's complement number representation.
 (d) ASCII Code.
 (e) Basic dynamic RAM Cell.

[Time: Three Hours]


[Marks:80]

- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three questions from remaining five questions.
 3. Assume suitable data wherever necessary.


Attempt the following:

20

- a. Find the value of I_1

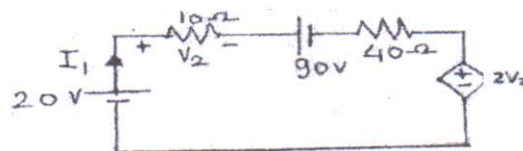

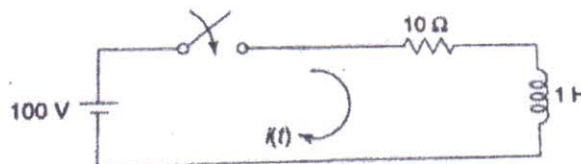- b. In the given network the switch is closed at $t = 0$. With zero current in the inductor find $i, \frac{di}{dt}$, at $t = 0^+$



- c. What are the advantages of an A.C. Bridge?
d. Obtain pole-zero plot of the following function

$$F(s) = \frac{s(s+2)}{(s+1)(s+3)}$$

- e. Explain construction and working of D'Arsonval Galvanometer.
f. Test whether polynomial is Hurwitz;
i) $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$
ii) $P(s) = s^5 + 3s^3 + 2s$


10
10

- g. State how you will derive the expression for frequency in case of Wien Bridge.
h. Explain construction and working of PMMC instrument.

10
10


- i. Find Thevenin's equivalent network

10

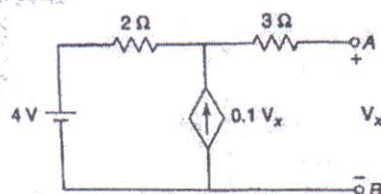


TURN OVER

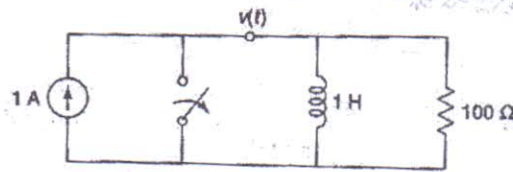
- b In the network shown in fig. At $t=0$, the switch is opened. Calculate v , $\frac{dv}{dt}$ at $t=0+$



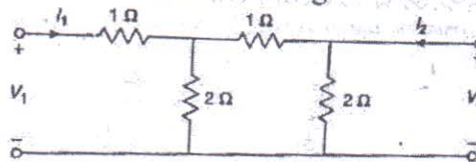- 5 a Obtain ABCD parameters for the network shown in fig.



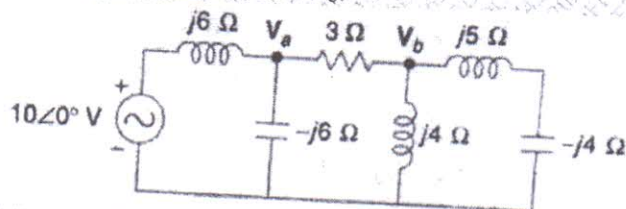- b In the network shown below determine V_a and V_b .



- 6 a What are Q meters and how do they work?
b For the network shown below, calculate the maximum power that may be dissipated in load resistor R_L

