


Please check whether you have got the right question paper.

- N.B:**
1. Question no1 is compulsory and solve any three questions from remaining.
 2. Draw neat and labeled diagrams.
 3. Assume suitable data if it is required.

Solve any five:

- 1) Draw the output waveform for following circuit. Identify the type.


20

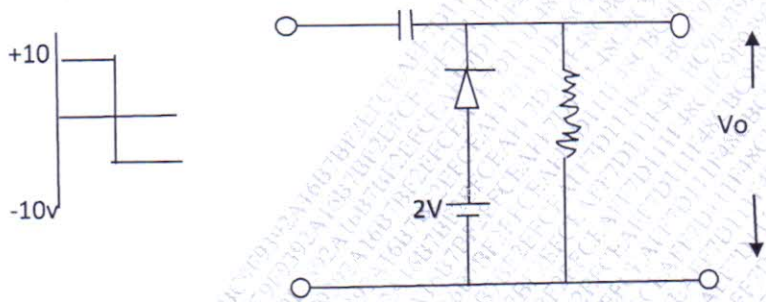

- 2) Explain any one biasing circuit used for E-MOSFET.
- 3) Explain effect of coupling and by pass capacitors on frequency response of CS amplifier.
- 4) State advantages of negative feedback.
- 5) Derive expression for efficiency of Class A Transformer coupled amplifier.
- 6) Compare CS amplifier with CE amplifier.

- a) For the given circuit find I_B , V_{CE} , I_{CQ} .


10

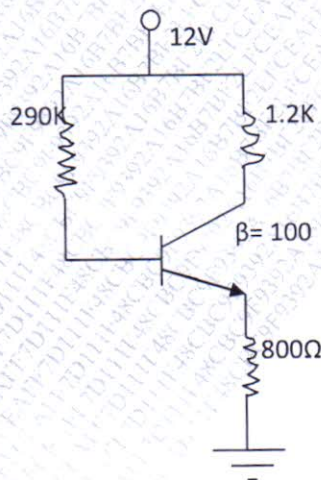

- b) Explain working of CS amplifier using JFET and derive formula for voltage gain, R_i and R_o . (using self bias)


10

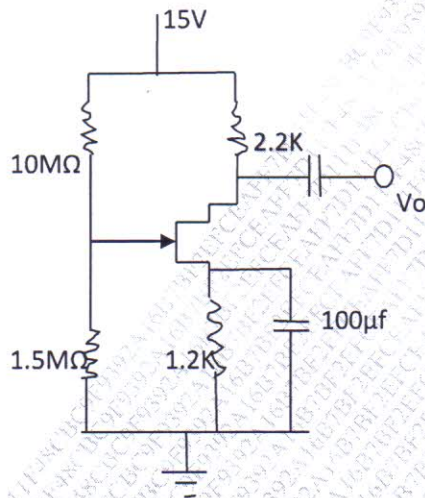- Q3 a) Explain need for cascading amplifier stages. Explain working of CS-CE multistage amplifier and Derive expressions for A_{VT} , R_i and R_o . 12
- b) Explain working of Wein Bridge oscillator with the help of circuit diagram and give equation of frequency of oscillations. 08
- Q4 a) For dual i/p balanced output diff amp derive expression for A_d and A_c . Suggest modification to improve CMRR. 10
- b) For the following circuit calculate A_v , R_i and R_o . 10



$I_{DSS}=8\text{mA}$, $V_p=3\text{V}$, $R_d=50\text{k}$

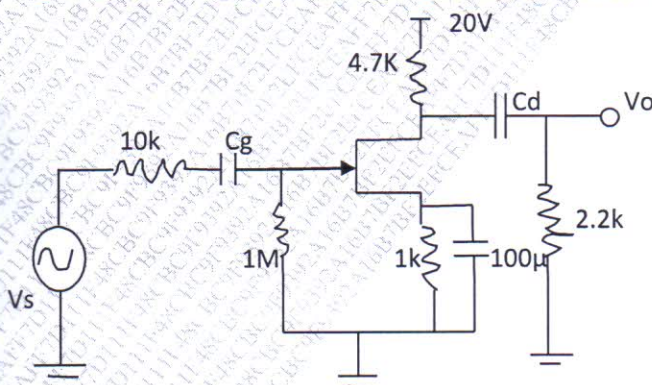- Q5 a) Prove that efficiency of Class B transformer coupled power amplifier is 78.5%. Suggest schemes For removing cross over distortion. 10
- b) For the given circuit of CS amplifier find higher cut off frequency. 10



$I_{DSS}=8\text{mA}$, $V_p=-4\text{V}$, $r_d=\infty$

$C_{gs}=2\text{pF}$, $C_{gs}=4\text{pF}$, $C_{ds}=0.5\text{pF}$, $c_{wi}=5\text{pF}$, $c_{wo}=6\text{pF}$

(c_{wi} & c_{wo} are wiring capacitances at i/p and o/p respectively.)

Q.6

Write short notes on any four:

20

- 1) Comparison of CB, CE and CC amplifier
 - 2) Current series negative feedback
 - 3) Constant current source (in diff amp)
 - 4) Cascode amplifier
 - 5) Heat sink used in power amplifiers.
-

Q.P. Code : 26077

[Time: 3 Hours]

[Marks: 80]

Please check whether you have got the right question paper.

- N.B:
1. Question No. 1 is compulsory.
 2. Attempt any three questions from remaining.
 3. Assume suitable data if required.
 4. Figure to the right indicate full marks.


1. Attempt **any four** from the following:

20

- a) Explain any five rules of root locus plot.
- b) What are the properties of state transition matrix.
- c) Explain adaptive control system.
- d) Describe the Mason's gain formula with an example.
- e) Explain need of compensators.

2. a) Obtain the overall transfer function from block diagram.

10

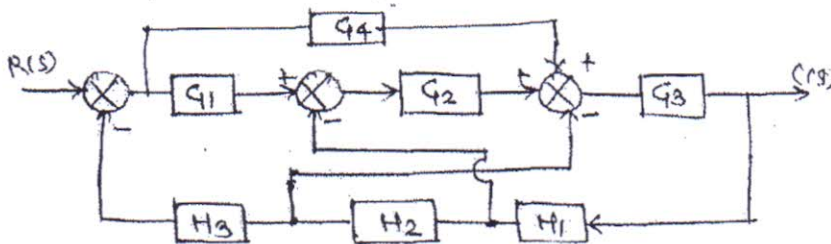

b) Find the solution of following state equation.

10

$$\dot{x} = \begin{bmatrix} -5 & -6 \\ 1 & 0 \end{bmatrix} x + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u$$

$$y = [1 \quad 1] x$$

3. a) Explain the type of signal which produces a finite steady state error for following system. Also find the steady state error.

10

i) $G(s)H(s) = \frac{20}{(s+2)(s+3)}$

ii) $G(s)H(s) = \frac{20(s+1)}{s^2(s+2)(s+4)}$


iii) $G(s)H(s) = \frac{2.5(s^2+2s+1)}{s(s+1)(s^2+5s+2)}$

b) Derive an Expression for output response of a second order under damped control system. Assume the input to be unit step signal.

10

Turn Over

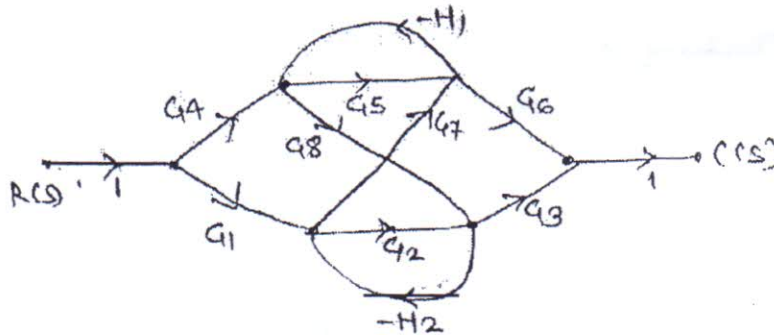4. a) Draw the root locus for the system with $G(s)H(s) = \frac{K(S+2)(S+3)}{S(S+1)}$ and comment on stability. 10
- b) Determine the stability of the system having characteristic equation $S^5 + S^4 + 2S^3 + 3S + 5 = 0$ 10
5. a) Draw Bode plot and find gain margin and phase margin for $G(s)H(s) = \frac{64(S+2)}{S(S+0.5)(S^2 + 3.2S + 64)}$ 10
- b) Discuss the stability of system using Nyquist plot for $G(s)H(s) = \frac{20}{S(S+4)(S-2)}$. 10
6. Attempt any two 20
- a) Different composite controllers.
- b) Co-relation between time domain and frequency domain specification.
- c) Using Mason's gain formula, find the gain of the following system in figure below.



Q.P. Code: 24863

Duration: 3 hrs.

Total marks: 60

N.B

1. Question 1 is compulsory
2. Solve any **THREE** out of the remaining 5 questions
3. Figures on the right indicate full marks
4. Assume suitable data if necessary

Q1. Solve any **THREE**

(15)

- a) A 6 pole, 50Hz Induction motor has a full load speed of 950 rpm. Calculate slip.
- b) Derive emf equation of a dc motor.
- c) State the important applications of brushless DC motor
- d) Explain v/f method of speed control of 3 phase induction motor

Q2. a) Develop equivalent circuit of a 3-phase Induction motor.

(8)

- b) Explain the working of capacitor start Induction motor.

(7)

Q3. a) Describe the construction and working principle of a variable reluctance motor.

(8)

- b) With neat diagram, discuss the working of a 3 point starter in a dc motor.

(7)

Q4. a) Name different types of unipolar brushless DC motor & describe any one type in detail

(8)

- b) What are the advantages, disadvantages & applications of Switched reluctance motors?

(7)

Q5. a) Compare 3 phase induction motor with 3 phase synchronous motor.

(7)

- b) Describe torque-slip characteristics of a three phase induction motor in 4 modes

(8)

Q6. Write short notes on

(15)

- a) Auto-transformer Starting of 3 phase induction motor
- b) Permanent magnet synchronous motor
- c) Double field revolving theory

Fundamentals of Communication Engineering

Q.P. Code :26508

[Time: 3 Hours]

[Marks:80]

Please check whether you have got the right question paper.

N.B: 1) Question 1 is compulsory and Solve any three from the remaining five questions

2) Assume suitable data if necessary.

3) Figures to the right indicate full marks.

- Q.1 Answer any **four** questions from the following: 20
- Explain the advantages and disadvantages of TRF receiver.
 - What is multiplexing? Compare TDM with FDM.
 - Discuss the need for modulation in wireless communication system.
 - What is AGC? Why is AGC needed in super heterodyne receivers?
 - Compare AM and FM.
- Q.2 a) With a neat circuit diagram and waveforms, explain the working of envelope detector. 04
What are its merits and demerits?
- b) A sinusoidal carrier has amplitude of 10v and frequency 30 KHz is amplitude modulated by a sinusoidal voltage of amplitude 3v and frequency 1 KHz. Modulated voltage is developed across a $50\ \Omega$ resistance. i) Write the equation for modulated wave and draw the modulated wave indicating V_{max} , V_{min} ii) Determine modulation Index. And calculate total power in the modulated wave iv) Draw the spectrum of modulated wave. 06
- c) Explain anyone type of SSB generation and detection with neat diagrams 10
- Q.3 a) With the help of a neat circuit diagram, explain the working of Foster Seeley discriminator. What is its disadvantage? 10
- b) With a neat block diagram, discuss the working of Linear Delta modulation, its advantages and disadvantages. 10
- Q.4 a) With a neat block diagram, explain the function of each block of Super heterodyne AM receiver. 10
- b) State Sampling theorem. Explain the two sampling techniques. What is aliasing error? How is it overcome? 10
- Q.5 a) Explain the terms with reference to Radio receivers: Selectivity, Sensitivity, Fidelity and Double spotting 10
- b) Discuss the generation and demodulation of PWM signal. For a sinusoidal modulating signal, draw PPM, and PWM pulses 10
- Q.6 Write short notes on any **four**:
- FM wave generation using Armstrong method
 - ISB Transmission
 - Pre emphasis and De emphasis circuits with waveforms
 - Skywave Propagation
 - Noise triangle
